



CMOS IC Application Note

S-19980/19990 Series FLYBACK CONVERTER CIRCUIT

Rev.1.0_00

© ABLIC Inc., 2024

This application note is a reference that explains the flyback converter circuit using the S-19980/19990 Series.
Refer to the datasheet for details and specs.

Contents

1. Overview	3
2. Specifications.....	3
3. Application Circuit.....	4
4. Characteristics (Typical Data)	5
4.1 Efficiency (η) vs. Output current (I_{OUT_ISO1}) ($T_a = +25^\circ\text{C}$)	5
4.2 Output voltage (V_{OUT}) vs. Output current (I_{OUT_ISO1}) ($T_a = +25^\circ\text{C}$)	5
4.3 Output voltage (V_{OUT}) vs. Input voltage (V_{IN}) ($T_a = +25^\circ\text{C}$)	6
4.4 Switching waveform ($V_{IN} = 12\text{ V}$, $T_a = +25^\circ\text{C}$).....	6
4.5 Power-on ($V_{IN} = 12\text{ V}$, $V_{IN} = V_{EN} = 0\text{ V} \rightarrow 12\text{ V}$, $T_a = +25^\circ\text{C}$)	7
4.6 Load transient response ($V_{IN} = 12\text{ V}$, $T_a = +25^\circ\text{C}$).....	7
4.7 Short-circuit protection ($V_{IN} = 12\text{ V}$, $T_a = +25^\circ\text{C}$).....	7
5. Circuit Diagram	8
6. Precautions	10
7. Related Sources.....	10

1. Overview

S-19980/19990 Series is an automotive step-up switching regulator controller. It can also be used for flyback converter circuits as an application circuit.

This application note shows an example of a flyback converter circuit that generates an isolated power supply from a 12 V power supply for the bias power supply of the inverter gate driver.

2. Specifications

Table 1 Example of Specifications

($V_{IN} = 12\text{ V}$, $T_a = 25^\circ\text{C}$ unless otherwise specified)

Item	Symbol	Condition	Min.	Typ.	Max.	Unit
Operating input voltage	V_{IN}	–	8	12	16	V
Output voltage	V_{OUT1}	–	–	4.7	–	V
Isolated output voltage	V_{OUT_ISO1}	–	–	18	–	V
Output current	I_{OUT1}	–	–	0.1	0.2	A
Isolated output current	I_{OUT_ISO1}	–	–	0.1	0.2	A
Oscillation frequency	f_{OSC}	–	–	400	–	kHz
Transformer characteristics (MinebeaMitsumi Inc. TR11-A-S)						
Primary inductance	L_p	–	–	6.0	–	μH
Turns ratio	$N_p:N_1:N_2$	–	–	1:0.83:3	–	–
DC resistance N_p	R_{DCp}	–	–	50.2	–	$\text{m}\Omega$
DC resistance N_1	R_{DC1}	–	–	82.8	–	$\text{m}\Omega$
DC resistance N_2	R_{DC2}	–	–	375	–	$\text{m}\Omega$
Saturation current	I_{sat}	–	–	2.2	–	A
Withstand voltage	V_{di}	AC, 1 minute	–	–	2000	V_{rms}
Leakage inductance	L_{LEAK}	Primary side	–	0.07	–	μH

Caution These constants will not guarantee successful operation. Perform thorough evaluation including the temperature characteristics with an actual application to set the constants.

3. Application Circuit

Figure 1 shows the application circuit of "Table 1 Example of Specifications".


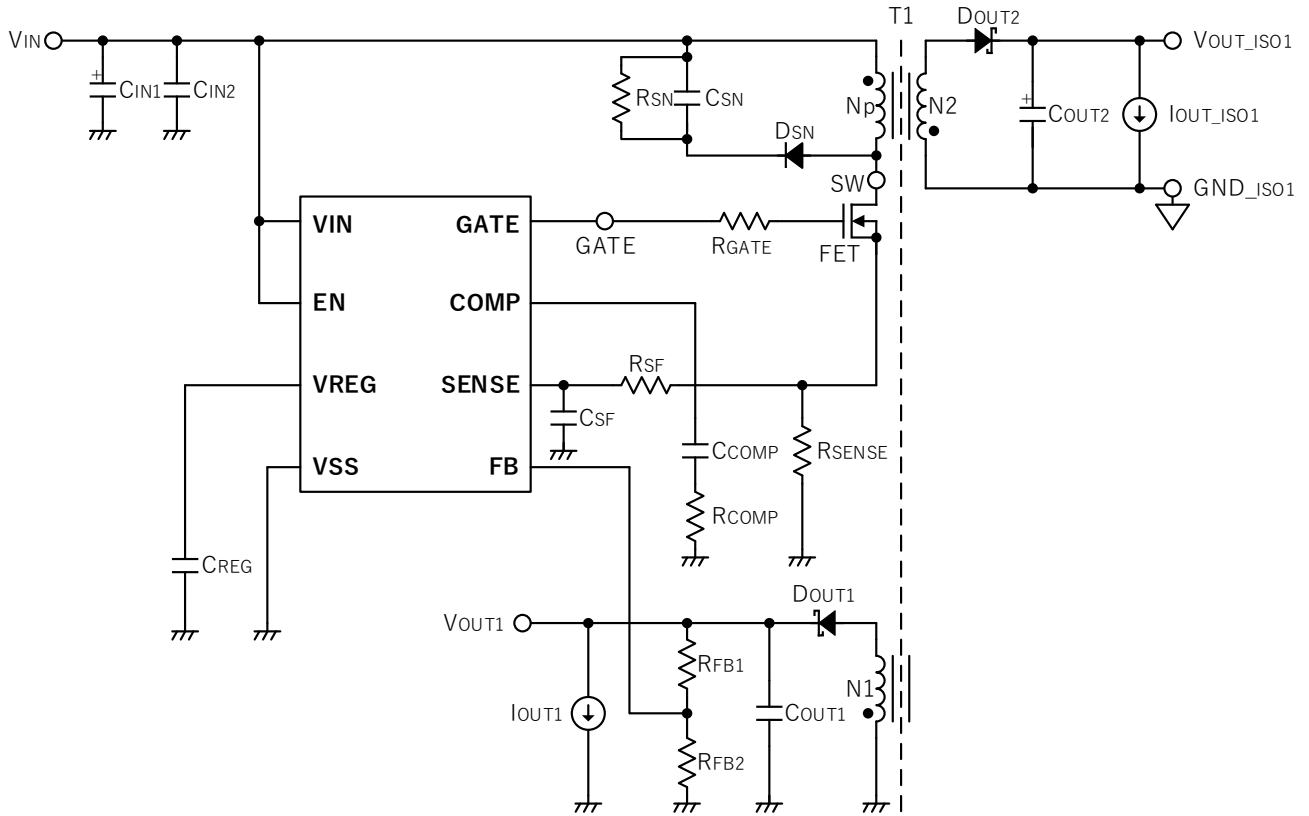


Figure 1

Caution It has not been confirmed whether the operation is normal or not in circuits other than the connection example. In addition, the connection example and the constants do not guarantee proper operation. Perform thorough evaluation using the actual application to set the constants.



4. Characteristics (Typical Data)

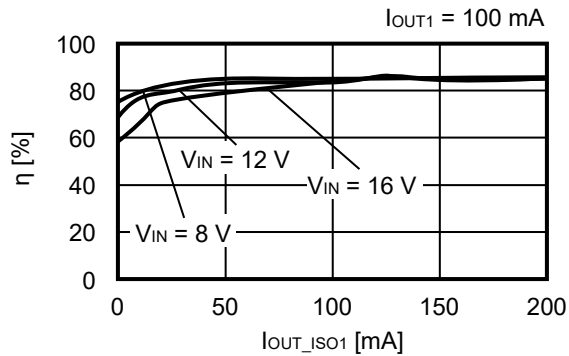4.1 Efficiency (η) vs. Output current (I_{OUT_ISO1}) ($T_a = +25^\circ\text{C}$)





4.2 Output voltage (V_{OUT}) vs. Output current (I_{OUT_ISO1}) ($T_a = +25^\circ\text{C}$)

4.2.1 $I_{OUT1} = 100\text{ mA}$

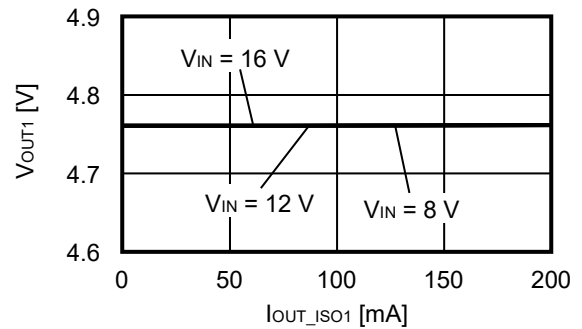
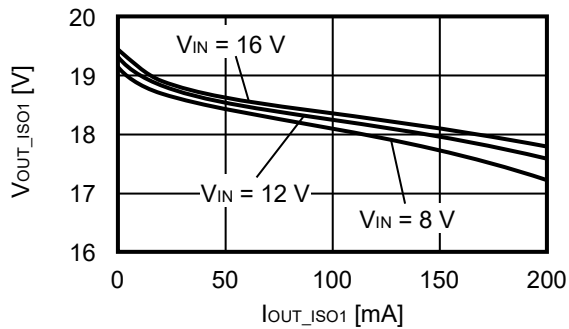


4.2.2 $I_{OUT1} = 150\text{ mA}$

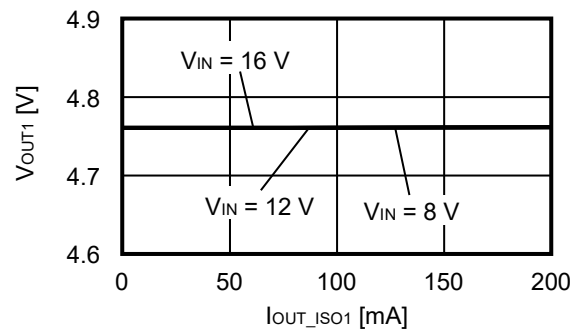
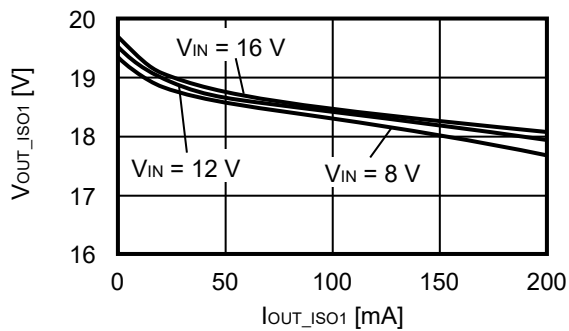


4.3 Output voltage (V_{OUT}) vs. Input voltage (V_{IN}) ($T_a = +25^\circ\text{C}$)

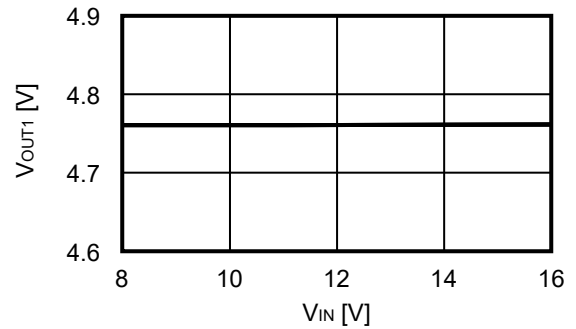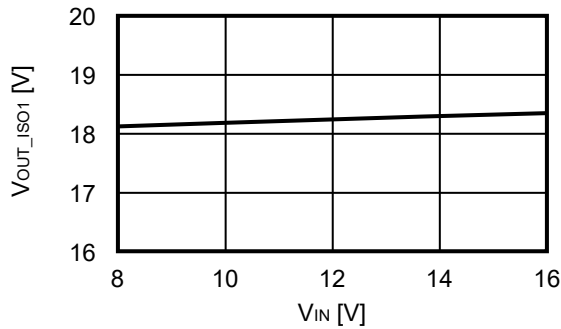4.3.1 $I_{OUT1} = 100\text{ mA}$, $I_{OUT_ISO1} = 100\text{ mA}$





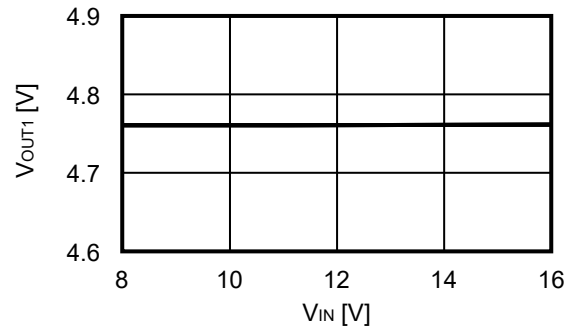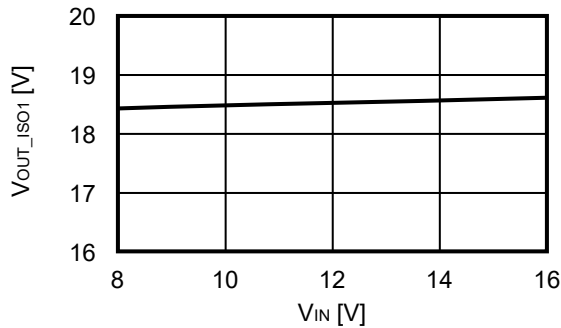4.3.2 $I_{OUT1} = 100\text{ mA}$, $I_{OUT_ISO1} = 50\text{ mA}$





4.4 Switching waveform ($V_{IN} = 12\text{ V}$, $T_a = +25^\circ\text{C}$)

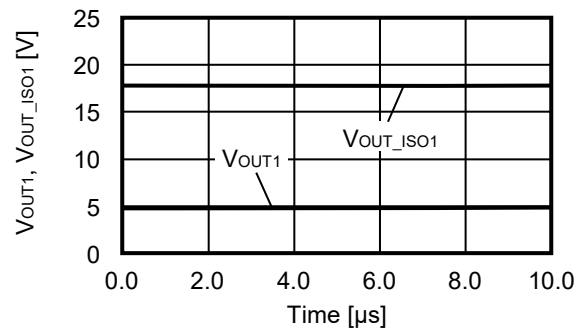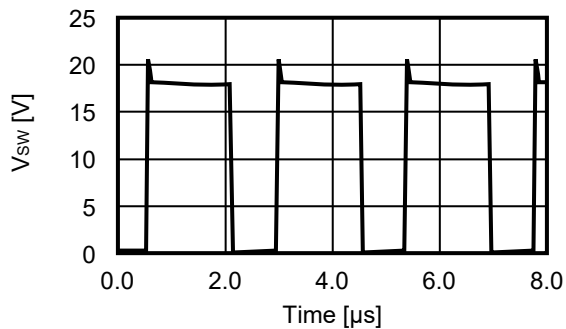4.4.1 $I_{OUT1} = 100\text{ mA}$, $I_{OUT_ISO1} = 150\text{ mA}$




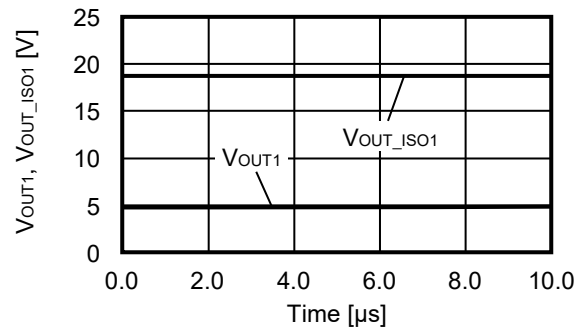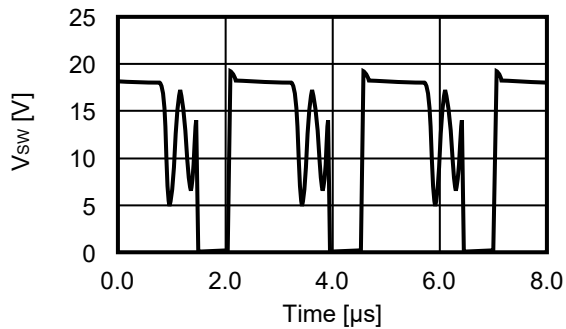4.4.2 $I_{OUT1} = 100\text{ mA}$, $I_{OUT_ISO1} = 50\text{ mA}$




4.5 Power-on ($V_{IN} = 12\text{ V}$, $V_{IN} = V_{EN} = 0\text{ V} \rightarrow 12\text{ V}$, $T_a = +25^\circ\text{C}$)

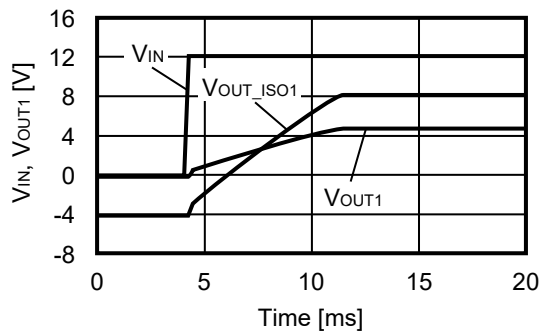4.5.1 $I_{OUT1} = 100\text{ mA}$, $I_{OUT_ISO1} = 150\text{ mA}$





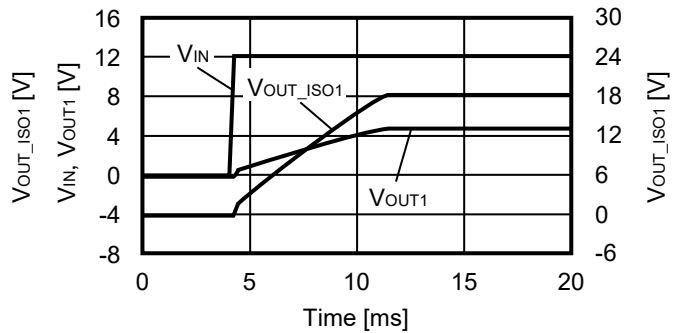4.5.2 $I_{OUT1} = 100\text{ mA}$, $I_{OUT_ISO1} = 50\text{ mA}$




4.6 Load transient response ($V_{IN} = 12\text{ V}$, $T_a = +25^\circ\text{C}$)

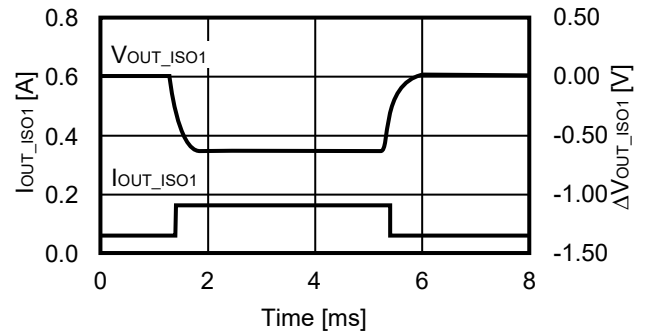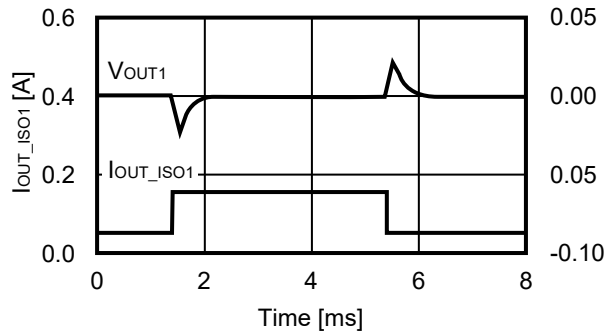4.6.1 $I_{OUT1} = 100\text{ mA}$, $I_{OUT_ISO1} = 50\text{ mA} \leftrightarrow 150\text{ mA}$



4.7 Short-circuit protection ($V_{IN} = 12\text{ V}$, $T_a = +25^\circ\text{C}$)

4.7.1 Hiccup control

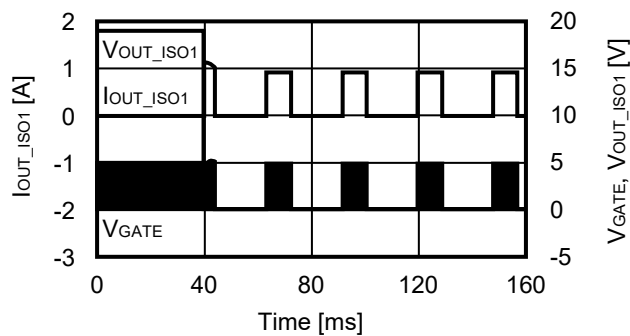

5. Circuit Diagram

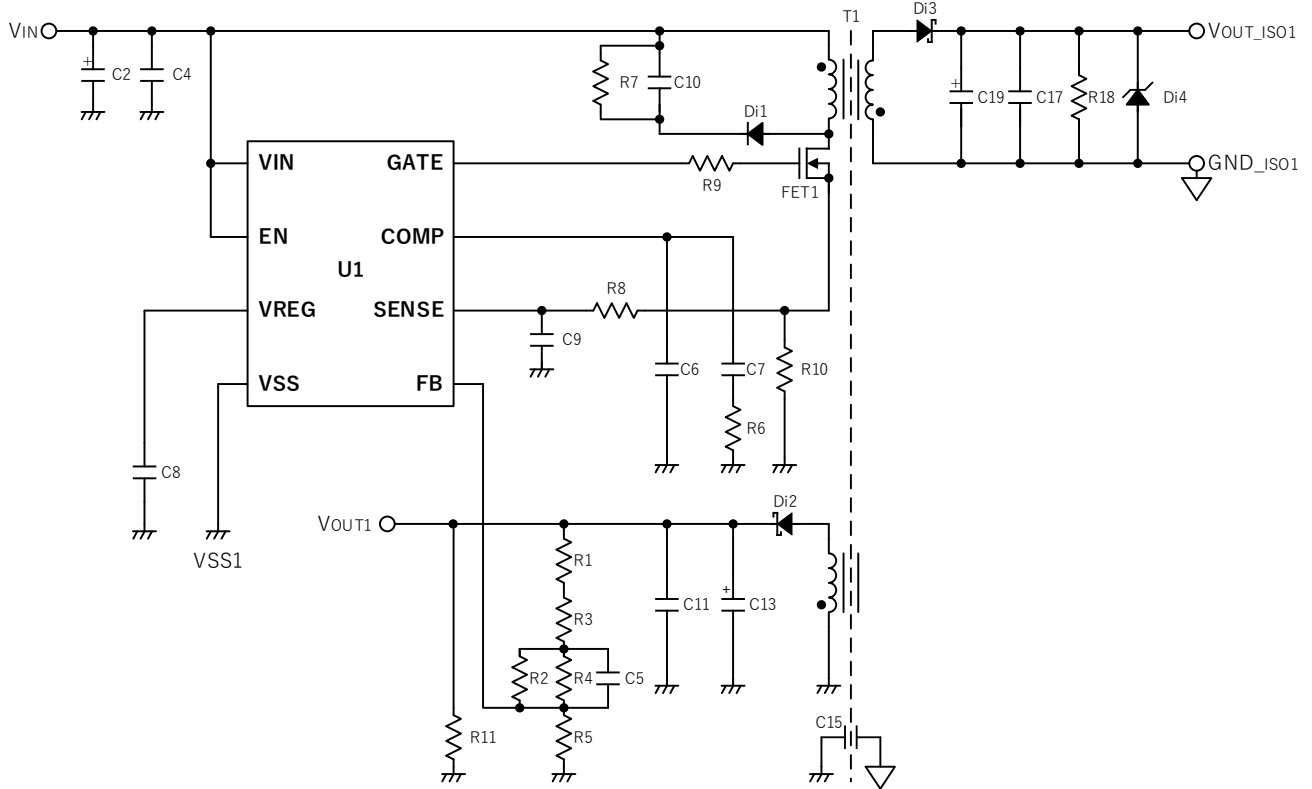


Figure 2 Circuit Diagram of the S-19980/19990 Series Flyback Converter Circuit

Table 2 shows external components used in the circuit diagram: Figure 2.

Table 2

Symbol	Value	Part Number	Manufacturer
U1	–	S-19990CA-S8T1U7	ABLIC Inc.
T1	–	TR11-A-S	MinebeaMitsumi Inc.
FET1	–	PMV60EN	Nexperia B.V.
Di1	–	ES1B-13-F	Vishay Intertechnology, Inc.
Di2, Di3	–	SS1P6LHM3	Vishay Intertechnology, Inc.
Di4	User settings	–	–
C2	33 μ F	GYC1H330MCQ1GS	NICHICON CORPORATION
C4	0.1 μ F	CGA4J2X8R1H104K	TDK Corporation
C5	User settings	–	–
C6	100 pF	CGA3E2NP01H101J	TDK Corporation
C7	4.7 nF	CGA3E2X8R1H472K	TDK Corporation
C8	1 μ F	CGA5L3X8R1H105K	TDK Corporation
C9	10 nF	CGA3E2X8R1H103K	TDK Corporation
C10	68 nF	CGA3E2X7R1H683K	TDK Corporation
C11	User settings	–	–
C13, C19	33 μ F	GYC1H330MCQ1GS	NICHICON CORPORATION
C15	1000 pF	1812GC102KAT1A	KYOCERA AVX Components Corporation
C17	User settings	–	–
R1	0 Ω	MCR3 series (1608)	ROHM CO., LTD.
R2	User settings	–	–
R3	3.9 k Ω	MCR3 series (1608)	ROHM CO., LTD.
R4	75 k Ω	MCR3 series (1608)	ROHM CO., LTD.
R5	16 k Ω	MCR3 series (1608)	ROHM CO., LTD.
R6	10 k Ω	MCR3 series (1608)	ROHM CO., LTD.
R7	15 k Ω	MCR3 series (6243)	ROHM CO., LTD.
R8	22 Ω	MCR3 series (1608)	ROHM CO., LTD.
R9	10 Ω	MCR3 series (1608)	ROHM CO., LTD.
R10	50 m Ω	ERJMB1SF50MU	Panasonic Industry Co., Ltd.
R11	User settings	–	–
R18	1 k Ω	MCR50 series (5025)	ROHM CO., LTD.

Caution 1. The constants may be changed without notice.

- 2.** It has not been confirmed whether the operation is normal or not in circuits other than the connection example. In addition, the connection example and the constants do not guarantee proper operation. Perform thorough evaluation using the actual application to set the constants.

6. Precautions

- The usages described in this application note are typical examples using ICs of ABLIC Inc. Perform thorough evaluation before use.
- Do not apply an electrostatic discharge to this IC that exceeds the performance ratings of the built-in electrostatic protection circuit.
- ABLIC Inc. claims no responsibility for any disputes arising out of or in connection with any infringement by products including this IC of patents owned by a third party.

7. Related Sources

Refer to the following datasheet for details of the S-19980/19990 Series.

S-19980 Series Datasheet

S-19990 Series Datasheet

The information described in this application note and the datasheet is subject to change without notice.

Contact our sales representatives for details.

Regarding the newest version of the datasheet, select product category and product name on our website, and download the PDF file.

www.ablic.com **ABLIC Inc. website**

Disclaimers (Handling Precautions)

1. All the information described herein (product data, specifications, figures, tables, programs, algorithms and application circuit examples, etc.) is current as of publishing date of this document and is subject to change without notice.
2. The circuit examples and the usages described herein are for reference only, and do not guarantee the success of any specific mass-production design.
ABLIC Inc. is not liable for any losses, damages, claims or demands caused by the reasons other than the products described herein (hereinafter "the products") or infringement of third-party intellectual property right and any other right due to the use of the information described herein.
3. ABLIC Inc. is not liable for any losses, damages, claims or demands caused by the incorrect information described herein.
4. Be careful to use the products within their ranges described herein. Pay special attention for use to the absolute maximum ratings, operation voltage range and electrical characteristics, etc.
ABLIC Inc. is not liable for any losses, damages, claims or demands caused by failures and / or accidents, etc. due to the use of the products outside their specified ranges.
5. Before using the products, confirm their applications, and the laws and regulations of the region or country where they are used and verify suitability, safety and other factors for the intended use.
6. When exporting the products, comply with the Foreign Exchange and Foreign Trade Act and all other export-related laws, and follow the required procedures.
7. The products are strictly prohibited from using, providing or exporting for the purposes of the development of weapons of mass destruction or military use. ABLIC Inc. is not liable for any losses, damages, claims or demands caused by any provision or export to the person or entity who intends to develop, manufacture, use or store nuclear, biological or chemical weapons or missiles, or use any other military purposes.
8. The products are not designed to be used as part of any device or equipment that may affect the human body, human life, or assets (such as medical equipment, disaster prevention systems, security systems, combustion control systems, infrastructure control systems, vehicle equipment, traffic systems, in-vehicle equipment, aviation equipment, aerospace equipment, and nuclear-related equipment), excluding when specified for in-vehicle use or other uses by ABLIC, Inc. Do not apply the products to the above listed devices and equipments.
ABLIC Inc. is not liable for any losses, damages, claims or demands caused by unauthorized or unspecified use of the products.
9. In general, semiconductor products may fail or malfunction with some probability. The user of the products should therefore take responsibility to give thorough consideration to safety design including redundancy, fire spread prevention measures, and malfunction prevention to prevent accidents causing injury or death, fires and social damage, etc. that may ensue from the products' failure or malfunction.
The entire system in which the products are used must be sufficiently evaluated and judged whether the products are allowed to apply for the system on customer's own responsibility.
10. The products are not designed to be radiation-proof. The necessary radiation measures should be taken in the product design by the customer depending on the intended use.
11. The products do not affect human health under normal use. However, they contain chemical substances and heavy metals and should therefore not be put in the mouth. The fracture surfaces of wafers and chips may be sharp. Be careful when handling these with the bare hands to prevent injuries, etc.
12. When disposing of the products, comply with the laws and ordinances of the country or region where they are used.
13. The information described herein contains copyright information and know-how of ABLIC Inc. The information described herein does not convey any license under any intellectual property rights or any other rights belonging to ABLIC Inc. or a third party. Reproduction or copying of the information from this document or any part of this document described herein for the purpose of disclosing it to a third-party is strictly prohibited without the express permission of ABLIC Inc.
14. For more details on the information described herein or any other questions, please contact ABLIC Inc.'s sales representative.
15. This Disclaimers have been delivered in a text using the Japanese language, which text, despite any translations into the English language and the Chinese language, shall be controlling.

2.4-2019.07