

CMOS IC Application Note

S-8204B Series Connection Examples

Rev.1.5_01

© ABLIC Inc., 2008-2016

The S-8204B Series is a protection IC for 3-series or 4-series cell lithium-ion rechargeable battery, and includes high-accuracy voltage detection circuits and delay circuits. By using cascade connection, it is also possible to protect 6-series or more cells lithium-ion rechargeable battery pack.

In case of protecting 5-series cell lithium-ion rechargeable battery pack, contact our sales office.


This application note is a guideline of the typical connection examples for applications using the S-8204B Series, and contains the components list.

Refer to the datasheet for details and spec of this IC.

It is possible to configure the following application by using the S-8204B Series.

- Protection circuit for multi-series cell of 3 cells or more

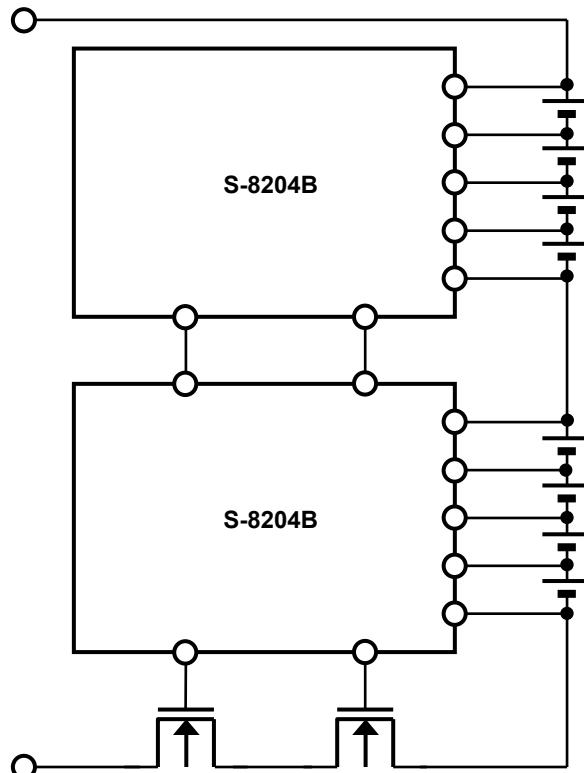• Protection circuit for multi-series cell using S-8204B Series




Contents

1. Protection circuit for 3-series / 4-series cell using S-8204B Series.....	3
1. 1 Protection circuit for 3-series cell (with discharge overcurrent protection function).....	3
1. 2 Protection circuit for 3-series cell (with discharge overcurrent protection function and automatic recovery function).....	4
1. 3 Protection circuit for 4-series cell (with discharge overcurrent protection function).....	5
1. 4 Protection circuit for 4-series cell (with discharge overcurrent protection function and automatic recovery function).....	6
1. 5 External components list (Protection circuit for 3-series / 4-series cell).....	7
2. Protection circuit for 6-series to 8-series cell using S-8204B Series (Cascade connection).....	8
2. 1 Protection circuit for 6-series cell (with discharge overcurrent protection function).....	8
2. 2 Protection circuit for 6-series cell (with discharge overcurrent protection function and automatic recovery function).....	9
2. 3 Protection circuit for 7-series cell (with discharge overcurrent protection function).....	10
2. 4 Protection circuit for 7-series cell (with discharge overcurrent protection function and automatic recovery function).....	11
2. 5 Protection circuit for 8-series cell (with discharge overcurrent protection function).....	12
2. 6 Protection circuit for 8-series cell (with discharge overcurrent protection function and automatic recovery function).....	13
2. 7 External components list (Protection circuit for 6-series to 8-series cell).....	14
3. Protection circuit for 9-series to 12-series cell using S-8204B Series (Cascade connection).....	16
3. 1 Protection circuit for 9-series cell (with discharge overcurrent protection function).....	16
3. 2 Protection circuit for 9-series cell (with discharge overcurrent protection function and automatic recovery function).....	17
3. 3 Protection circuit for 10-series cell (with discharge overcurrent protection function).....	18
3. 4 Protection circuit for 10-series cell (with discharge overcurrent protection function and automatic recovery function).....	19
3. 5 Protection circuit for 11-series cell (with discharge overcurrent protection function).....	20
3. 6 Protection circuit for 11-series cell (with discharge overcurrent protection function and automatic recovery function).....	21
3. 7 Protection circuit for 12-series cell (with discharge overcurrent protection function).....	22
3. 8 Protection circuit for 12-series cell (with discharge overcurrent protection function and automatic recovery function).....	23
3. 9 External components list (Protection circuit for 9-series to 12-series cell).....	24
4. Withstand voltage protection when S-8204B Series devices are connected in cascade	26
5. Precautions	27
6. Related source	27

1. Protection circuit for 3-series / 4-series cell using S-8204B Series

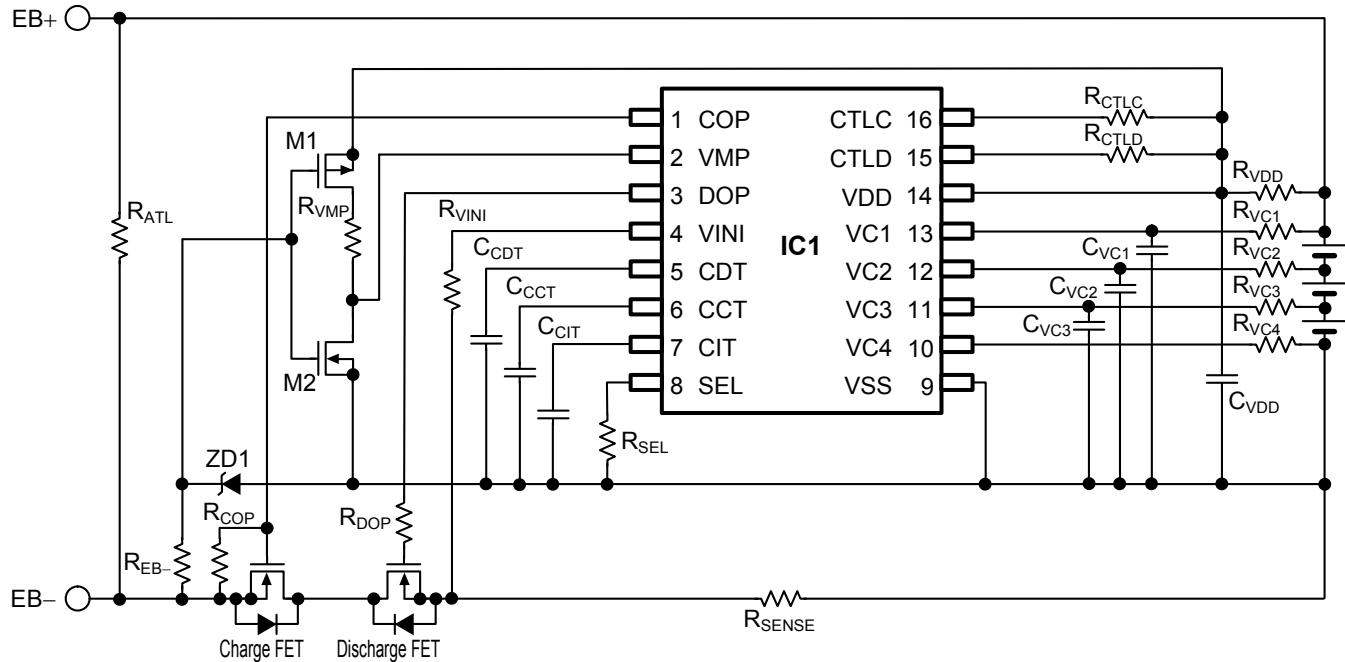1.1 Protection circuit for 3-series cell (with discharge overcurrent protection function)



Remark Refer to "1.5 External components list (Protection circuit for 3-series / 4-series cell)" for constants of external components.


Figure 1

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

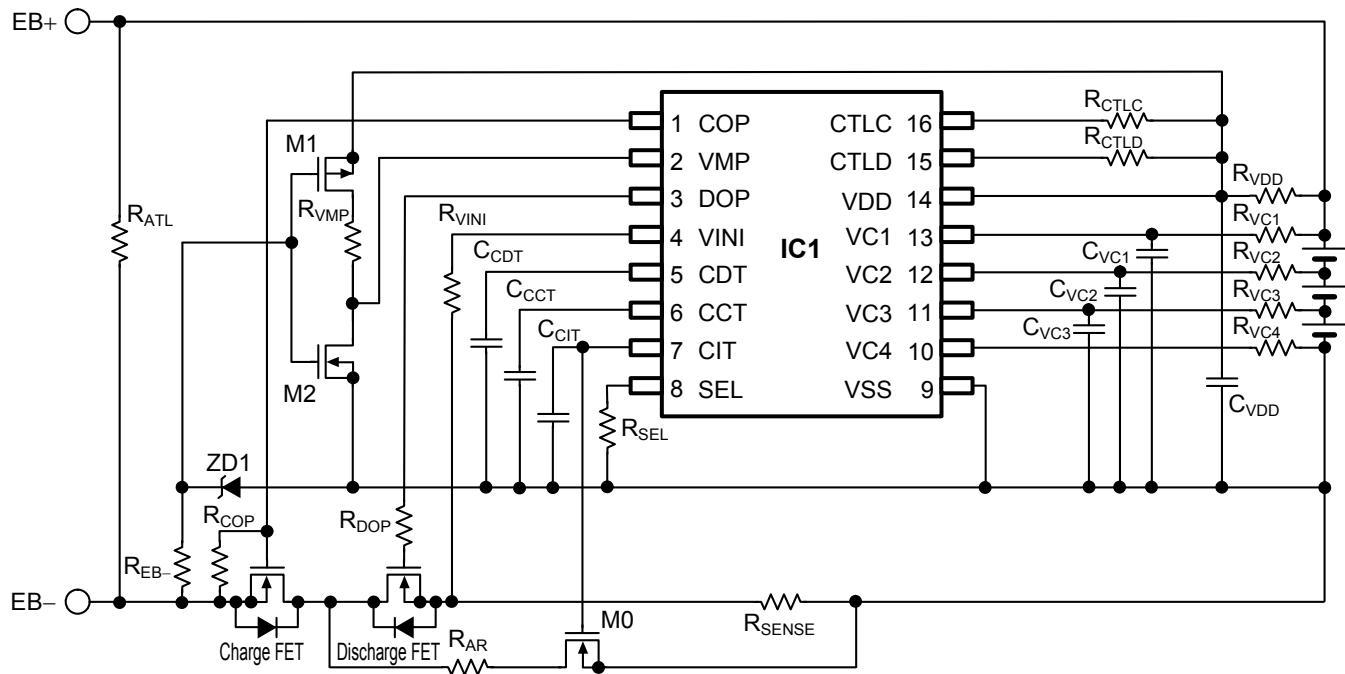1. 2 Protection circuit for 3-series cell

(with discharge overcurrent protection function and automatic recovery function)




Remark Refer to "1. 5 External components list (Protection circuit for 3-series / 4-series cell)" for constants of external components.

Figure 2

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

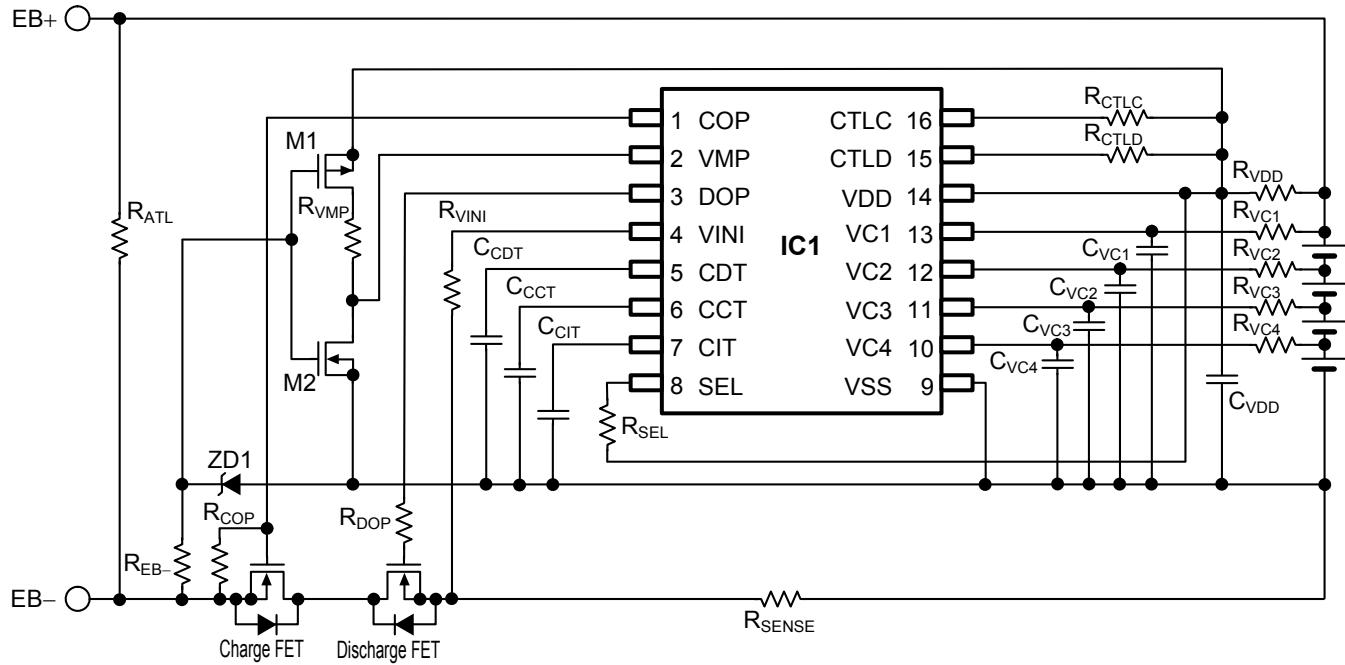1.3 Protection circuit for 4-series cell (with discharge overcurrent protection function)



Remark Refer to "1.5 External components list (Protection circuit for 3-series / 4-series cell)" for constants of external components.


Figure 3

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

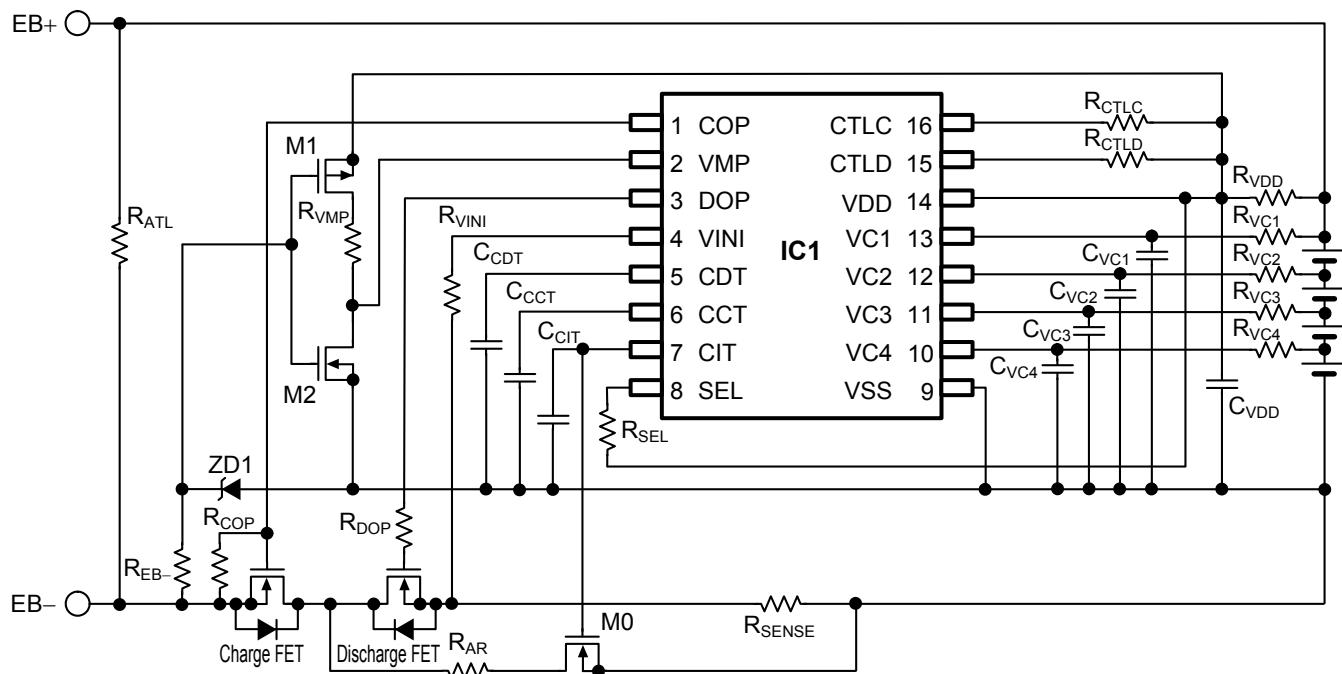1. 4 Protection circuit for 4-series cell

(with discharge overcurrent protection function and automatic recovery function)



Remark Refer to "1. 5 External components list (Protection circuit for 3-series / 4-series cell)" for constants of external components.

Figure 4

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

1. 5 External components list (Protection circuit for 3-series / 4-series cell)

Table 1 shows external components in the connection examples of Figure 1 to Figure 4.

Table 1


Symbol	Typical	Unit	Components Name	Maker	Note
IC1	–	–	S-8204B	ABLIC Inc.	Necessary
Rvc1	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc2	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc3	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc4	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Cvc1	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc2	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc3	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc4	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Rvdd	47	Ω	MCR03	ROHM CO., LTD.	Recommend
Cvdd	1	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Rsel	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Ccct	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Ccdt	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Ccit	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Rvini	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rctlc	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rctld	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rcop	1	MΩ	MCR03	ROHM CO., LTD.	Recommend
Rdop	5.1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvmp	5.1	kΩ	MCR03	ROHM CO., LTD.	Necessary
Rsense	–	–	–	–	–
M0	–	–	2SK1590C	Renesas Electronics Corporation	Recommend
M1	–	–	2SJ210C	Renesas Electronics Corporation	Recommend
M2	–	–	2SK1590C	Renesas Electronics Corporation	Recommend
ZD1	–	–	UDZS18B	ROHM CO., LTD.	Recommend
Rar	100	kΩ	MCR03	ROHM CO., LTD.	Recommend
Reb	1	MΩ	MCR03	ROHM CO., LTD.	Necessary
Ratl	20	MΩ	MCR03	ROHM CO., LTD.	Recommend
Charge FET	–	–	–	–	–
Discharge FET	–	–	–	–	–

Caution 1. The above constants are subject to change without prior notice.

2. These constants will not guarantee successful operation. Perform thorough evaluation using the actual application to set the constant.

2. Protection circuit for 6-series to 8-series cell using S-8204B Series (Cascade connection)

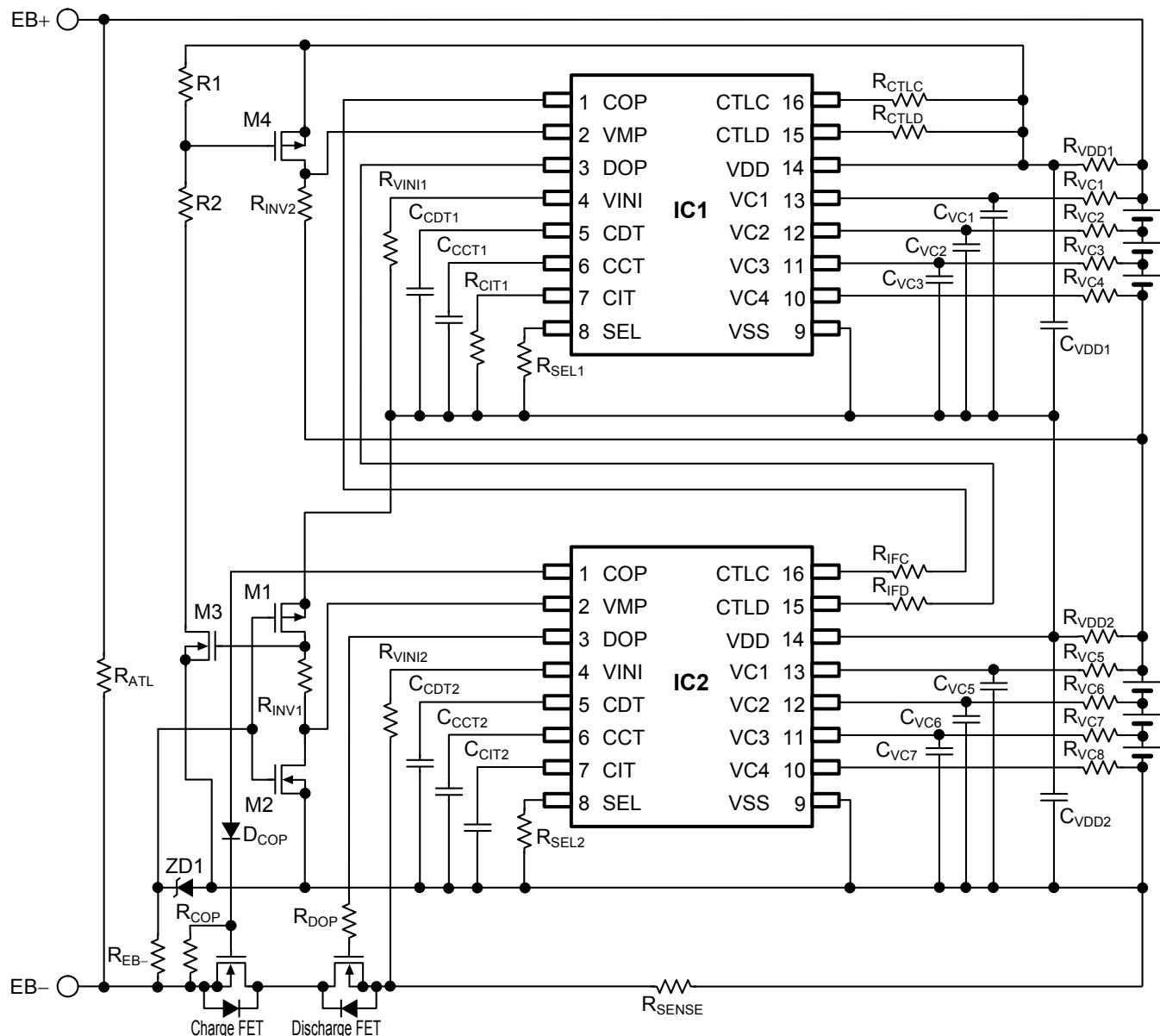2. 1 Protection circuit for 6-series cell (with discharge overcurrent protection function)



Remark Refer to "2. 7 External components list (Protection circuit for 6-series to 8-series cell)" for constants of external components.


Figure 5

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

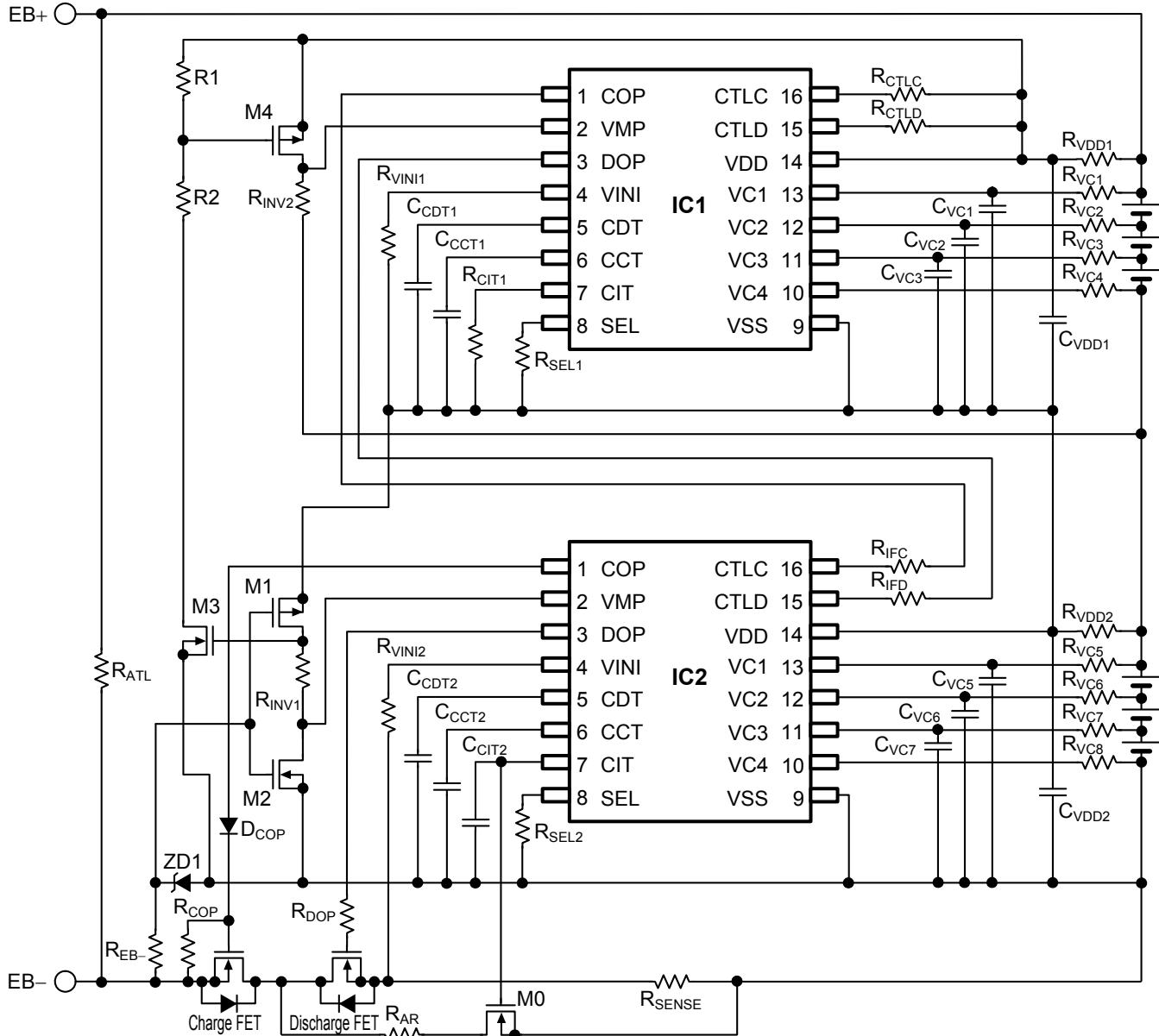2. 2 Protection circuit for 6-series cell

(with discharge overcurrent protection function and automatic recovery function)




Remark Refer to "2. 7 External components list (Protection circuit for 6-series to 8-series cell)" for constants of external components.

Figure 6

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

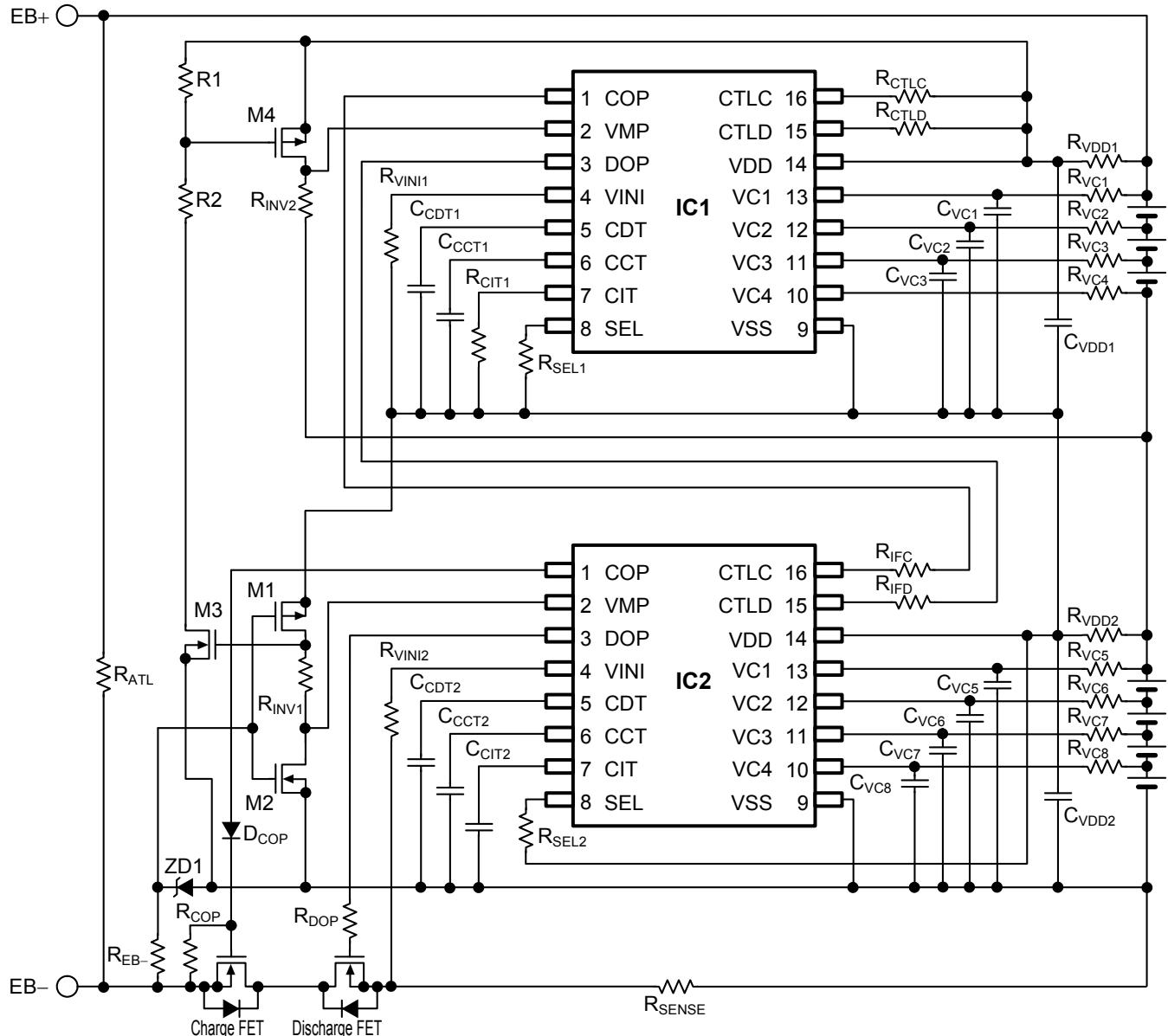2. 3 Protection circuit for 7-series cell (with discharge overcurrent protection function)



Remark Refer to "2. 7 External components list (Protection circuit for 6-series to 8-series cell)" for constants of external components.


Figure 7

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

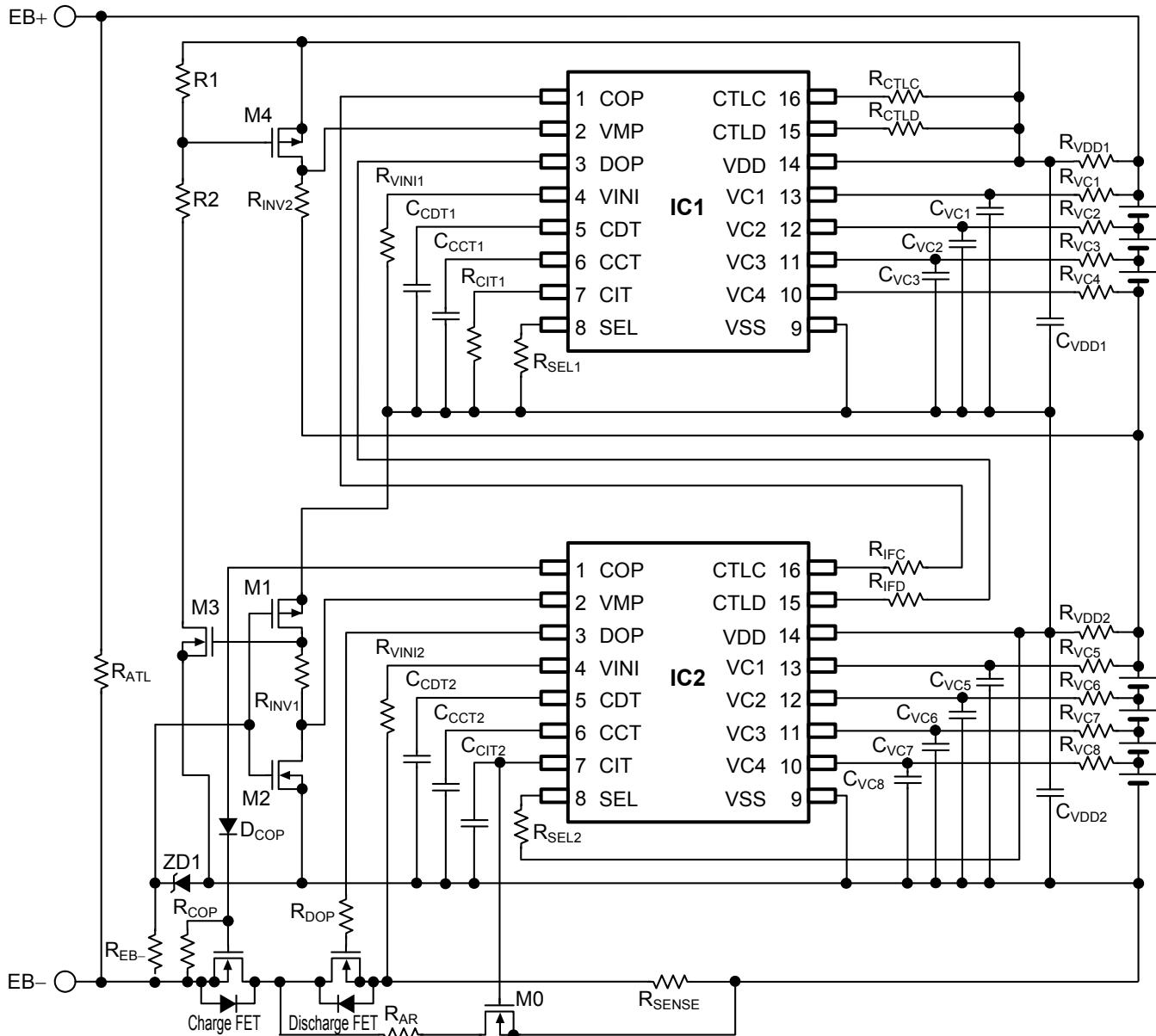2. 4 Protection circuit for 7-series cell

(with discharge overcurrent protection function and automatic recovery function)




Remark Refer to "2. 7 External components list (Protection circuit for 6-series to 8-series cell)" for constants of external components.

Figure 8

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

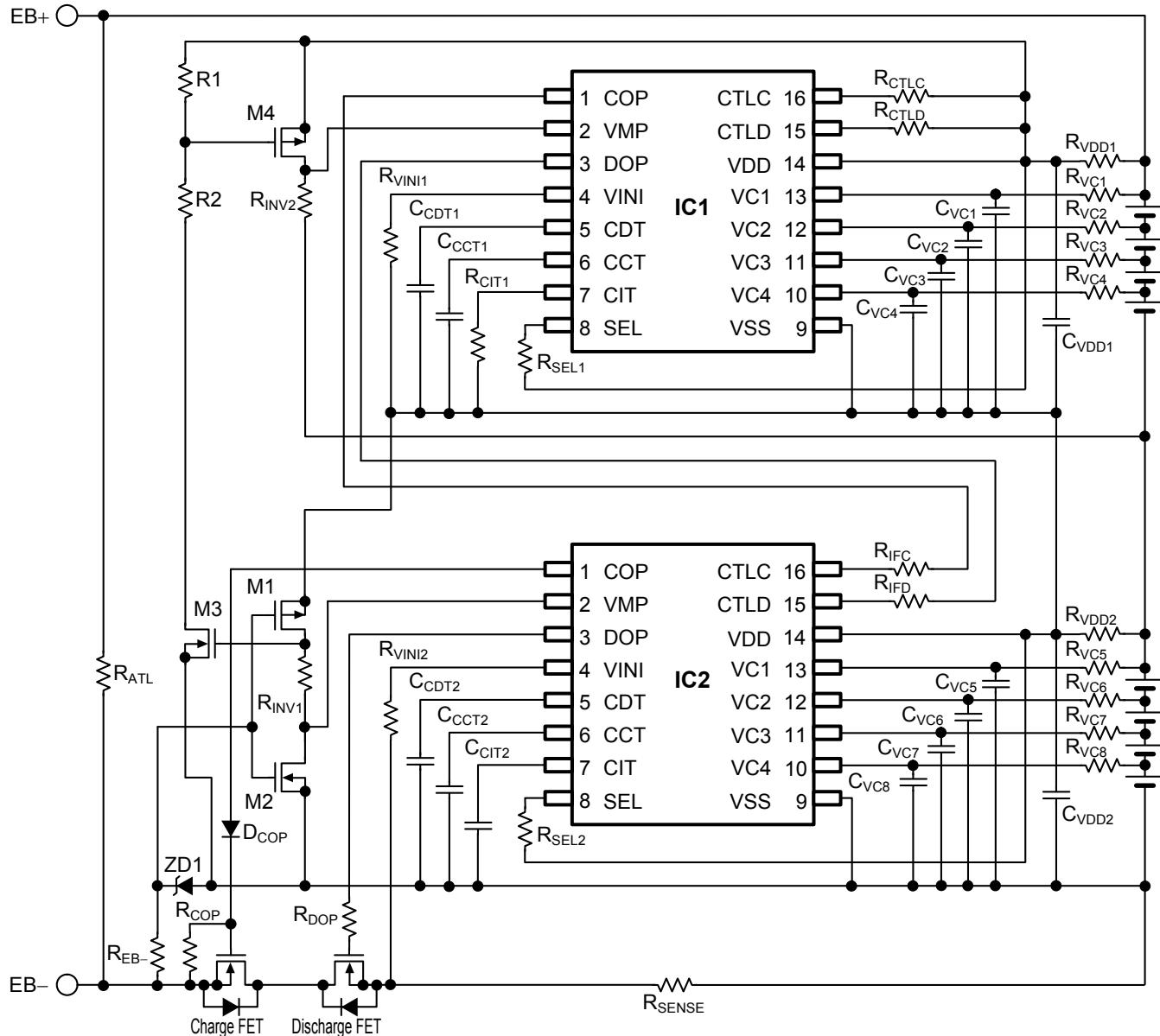2. 5 Protection circuit for 8-series cell (with discharge overcurrent protection function)



Remark Refer to "2. 7 External components list (Protection circuit for 6-series to 8-series cell)" for constants of external components.


Figure 9

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

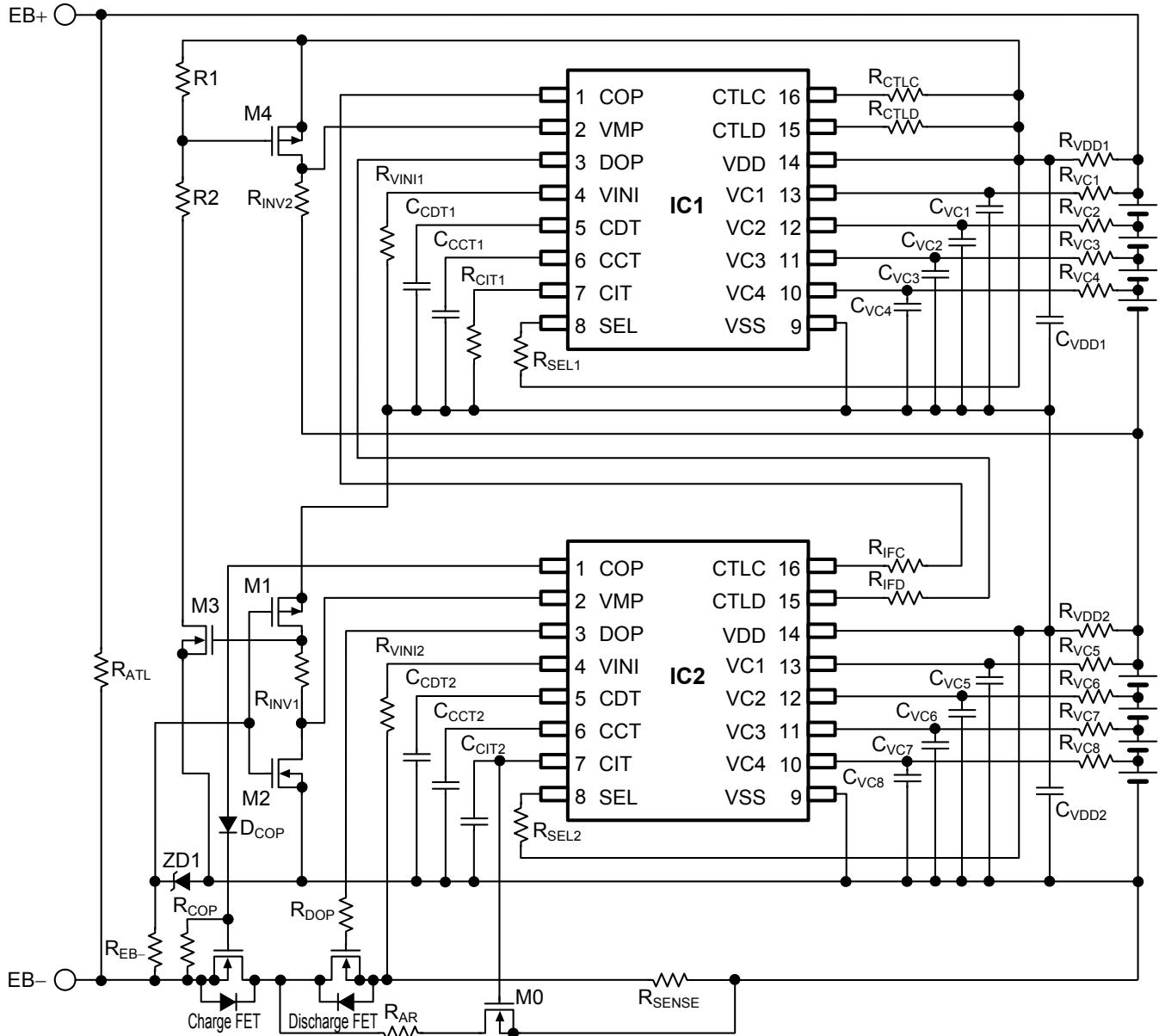2. 6 Protection circuit for 8-series cell

(with discharge overcurrent protection function and automatic recovery function)



Remark Refer to "2. 7 External components list (Protection circuit for 6-series to 8-series cell)" for constants of external components.

Figure 10

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

2. 7 External components list (Protection circuit for 6-series to 8-series cell)

Table 2 shows external components in the connection examples of **Figure 5** to **Figure 10**.

Table 2 (1 / 2)

Symbol	Typical	Unit	Components Name	Maker	Note
IC1	–	–	S-8204B	ABLIC Inc.	Necessary
IC2	–	–	S-8204B	ABLIC Inc.	Necessary
Rvc1	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc2	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc3	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc4	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc5	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc6	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc7	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvc8	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Cvc1	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc2	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc3	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc4	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc5	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc6	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc7	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvc8	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Rvdd1	47	Ω	MCR03	ROHM CO., LTD.	Recommend
Rvdd2	47	Ω	MCR03	ROHM CO., LTD.	Recommend
Cvdd1	1	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
Cvdd2	1.5	μF	GRM32D	Murata Manufacturing Co., Ltd.	Recommend
Rsel1	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rsel2	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Ccct1	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Ccct2	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Ccdt1	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Ccdt2	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Rcit1	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Ccit2	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
Rvini1	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rvini2	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rctlc	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rctld	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
Rifc	5.1	MΩ	MCR03	ROHM CO., LTD.	Necessary
Rifd	5.1	MΩ	MCR03	ROHM CO., LTD.	Necessary
Rinv1	5.1	kΩ	MCR03	ROHM CO., LTD.	Necessary
Rinv2	1	MΩ	MCR03	ROHM CO., LTD.	Necessary
Rcop	1	MΩ	MCR03	ROHM CO., LTD.	Recommend
Rdop	51	kΩ	MCR03	ROHM CO., LTD.	Recommend
Dcop	–	–	1SS355	ROHM CO., LTD.	Recommend
Rsense	–	–	–	–	–


Table 2 (2 / 2)

Symbol	Typical	Unit	Components Name	Maker	Note
M0	–	–	2SK1590C	Renesas Electronics Corporation	Recommend
M1	–	–	2SJ210C	Renesas Electronics Corporation	Recommend
M2	–	–	2SK1590C	Renesas Electronics Corporation	Recommend
M3	–	–	2SK1590C	Renesas Electronics Corporation	Recommend
M4	–	–	2SJ210C	Renesas Electronics Corporation	Recommend
ZD1	–	–	UDZS18B	ROHM CO., LTD.	Recommend
R1	10	MΩ	MCR03	ROHM CO., LTD.	Recommend
R2	10	MΩ	MCR03	ROHM CO., LTD.	Recommend
R _{AR}	100	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{EB}	1	MΩ	MCR03	ROHM CO., LTD.	Necessary
R _{ATL}	20	MΩ	MCR03	ROHM CO., LTD.	Recommend
Charge FET	–	–	–	–	–
Discharge FET	–	–	–	–	–

Caution 1. The above constants are subject to change without prior notice.
 2. These constants will not guarantee successful operation. Perform thorough evaluation using the actual application to set the constants.

3. Protection circuit for 9-series to 12-series cell using S-8204B Series (Cascade connection)

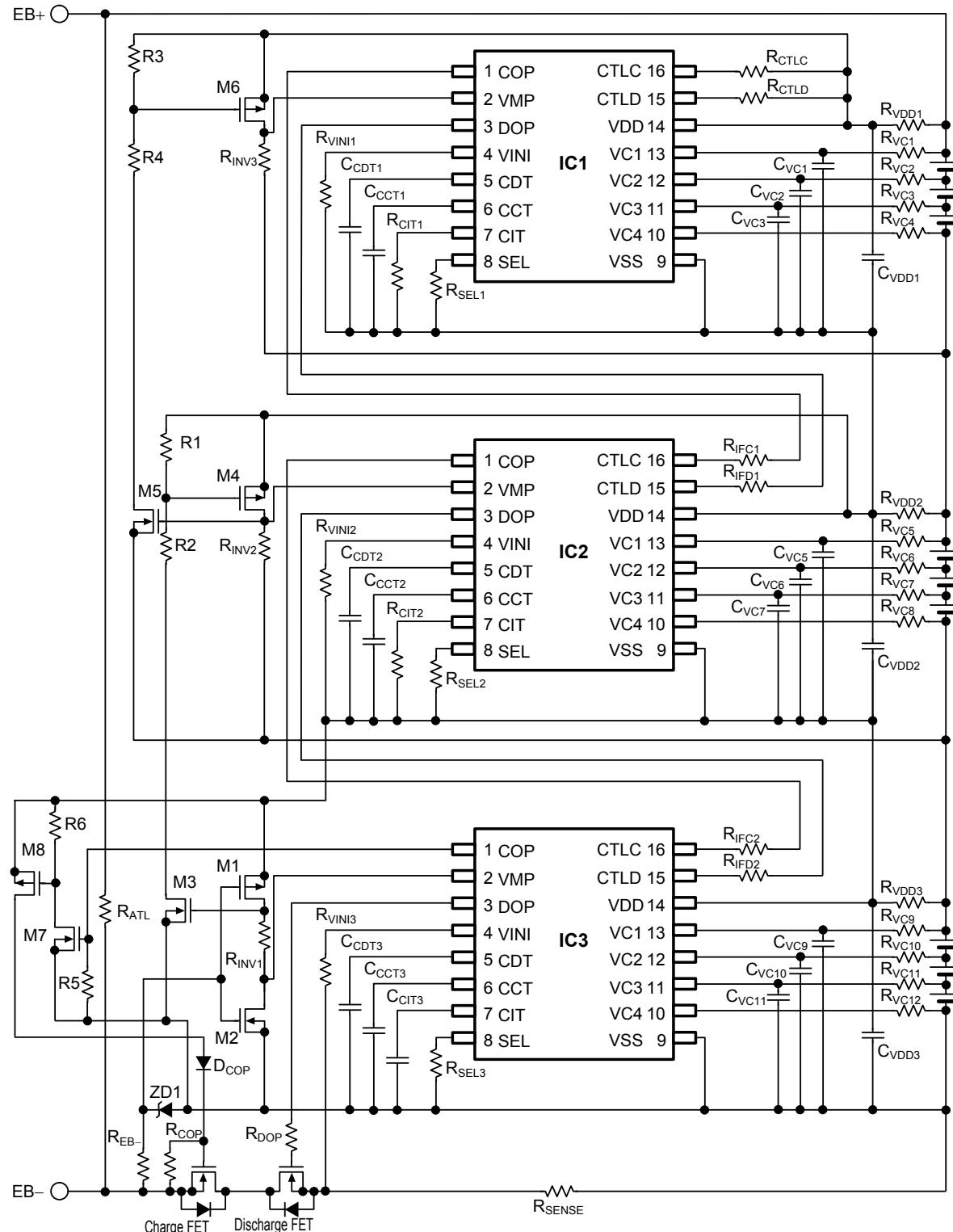3. 1 Protection circuit for 9-series cell (with discharge overcurrent protection function)



Remark Refer to "3. 9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.


Figure 11

Caution 1. The above example connection may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

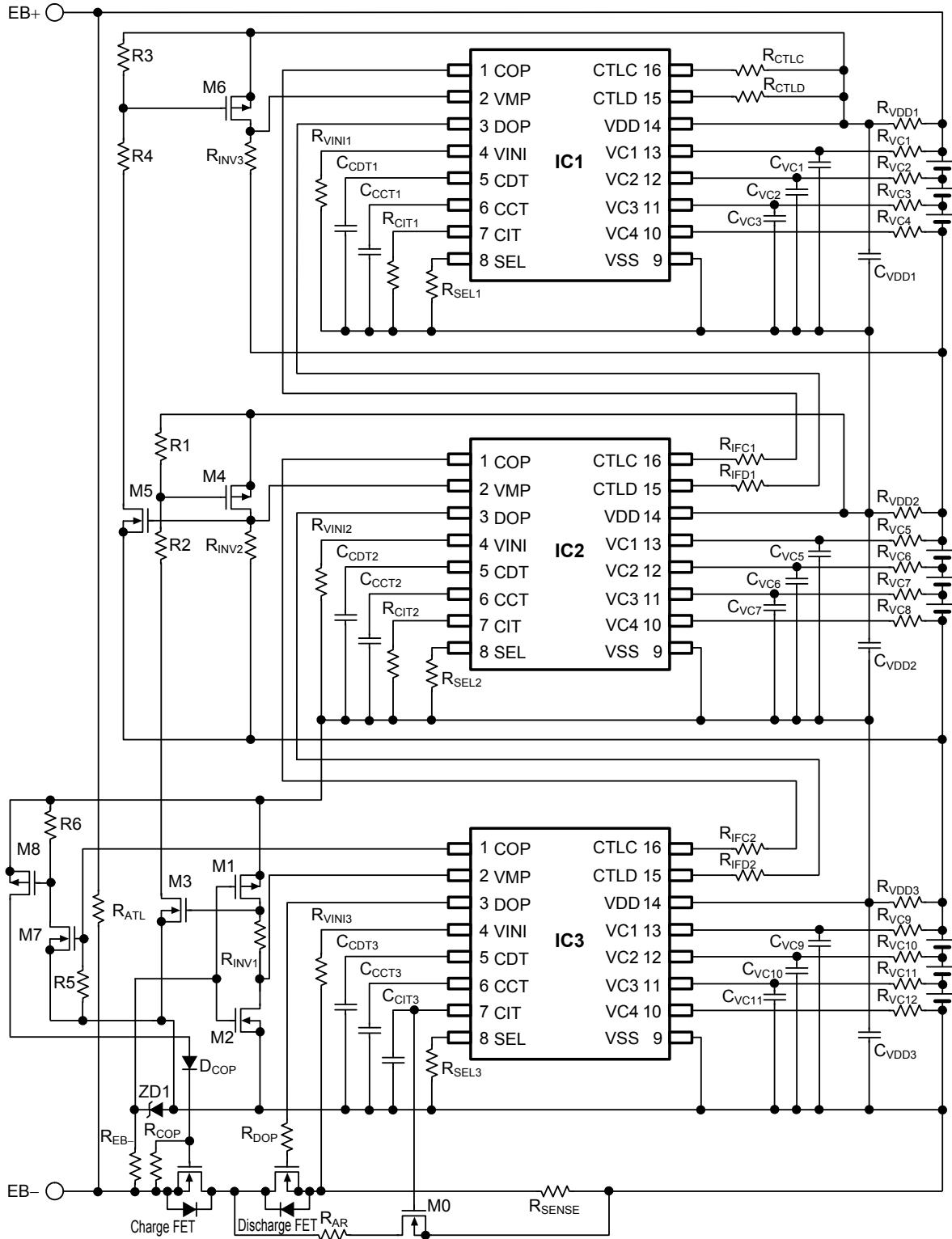3. 2 Protection circuit for 9-series cell

(with discharge overcurrent protection function and automatic recovery function)




Remark Refer to "3. 9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.

Figure 12

Caution 1. The above example connection may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

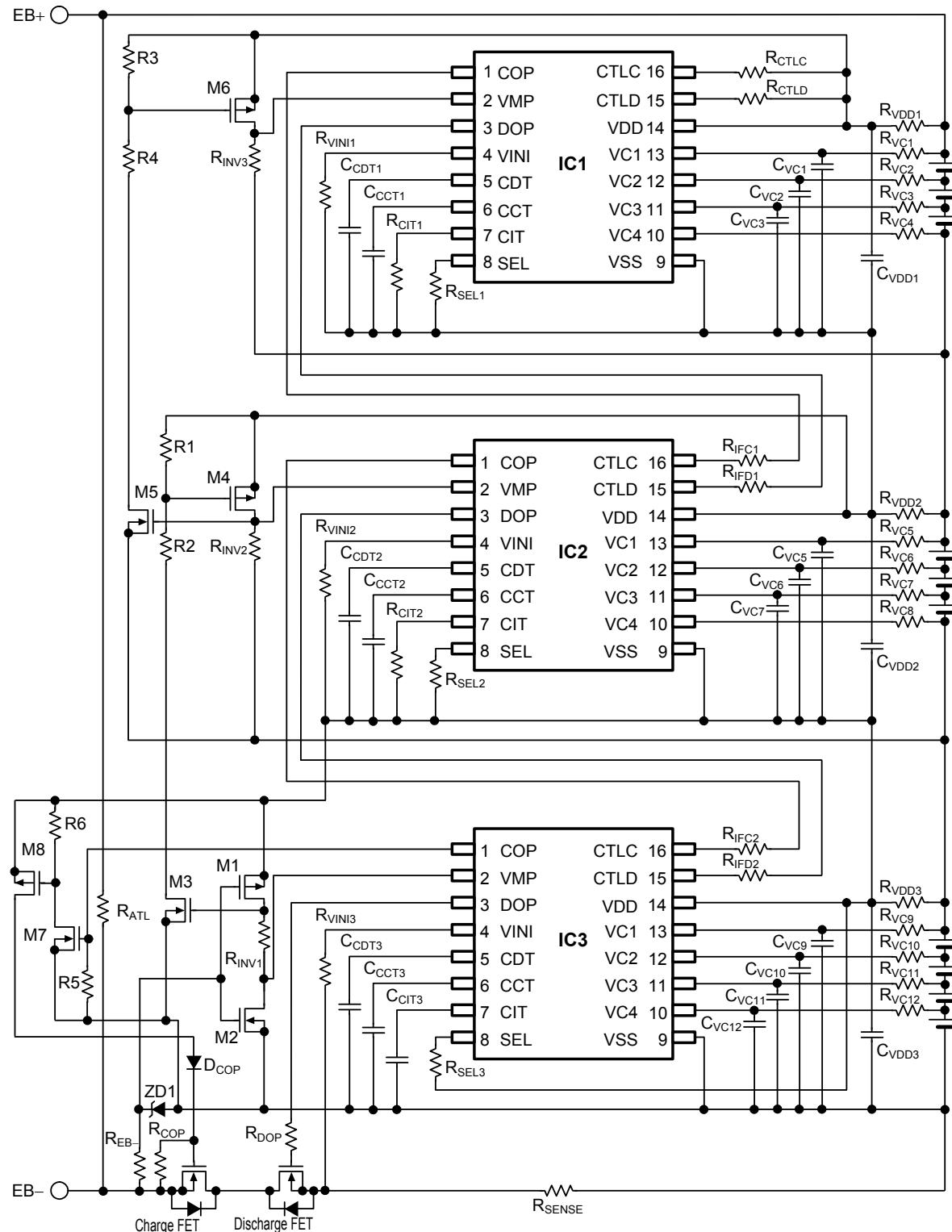3. 3 Protection circuit for 10-series cell (with discharge overcurrent protection function)




Remark Refer to "3. 9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.

Figure 13

- Caution 1.** The above connection example may be changed without notice.
2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

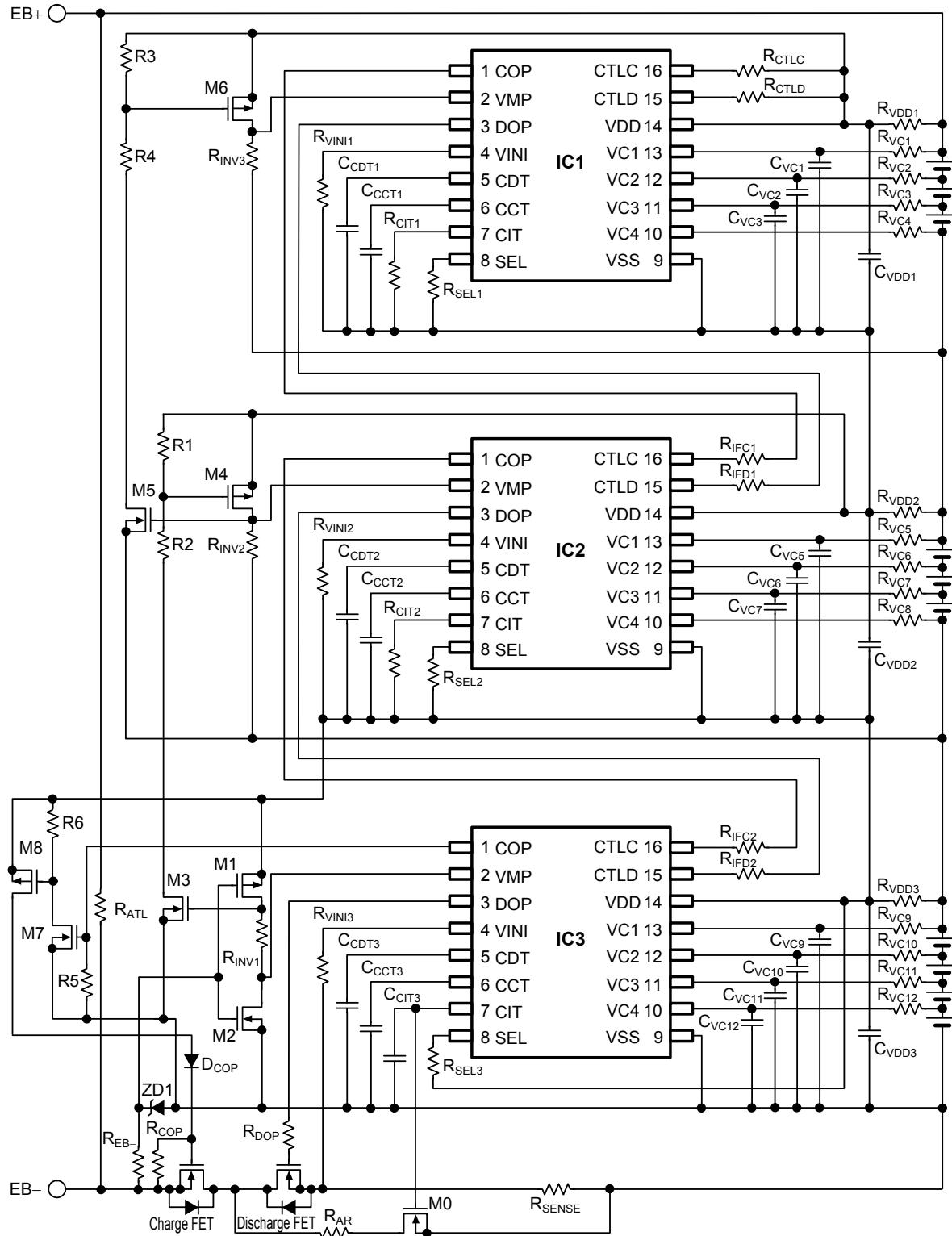**3. 4 Protection circuit for 10-series cell
(with discharge overcurrent protection function and automatic recovery function)**




Remark Refer to "3. 9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.

Figure 14

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

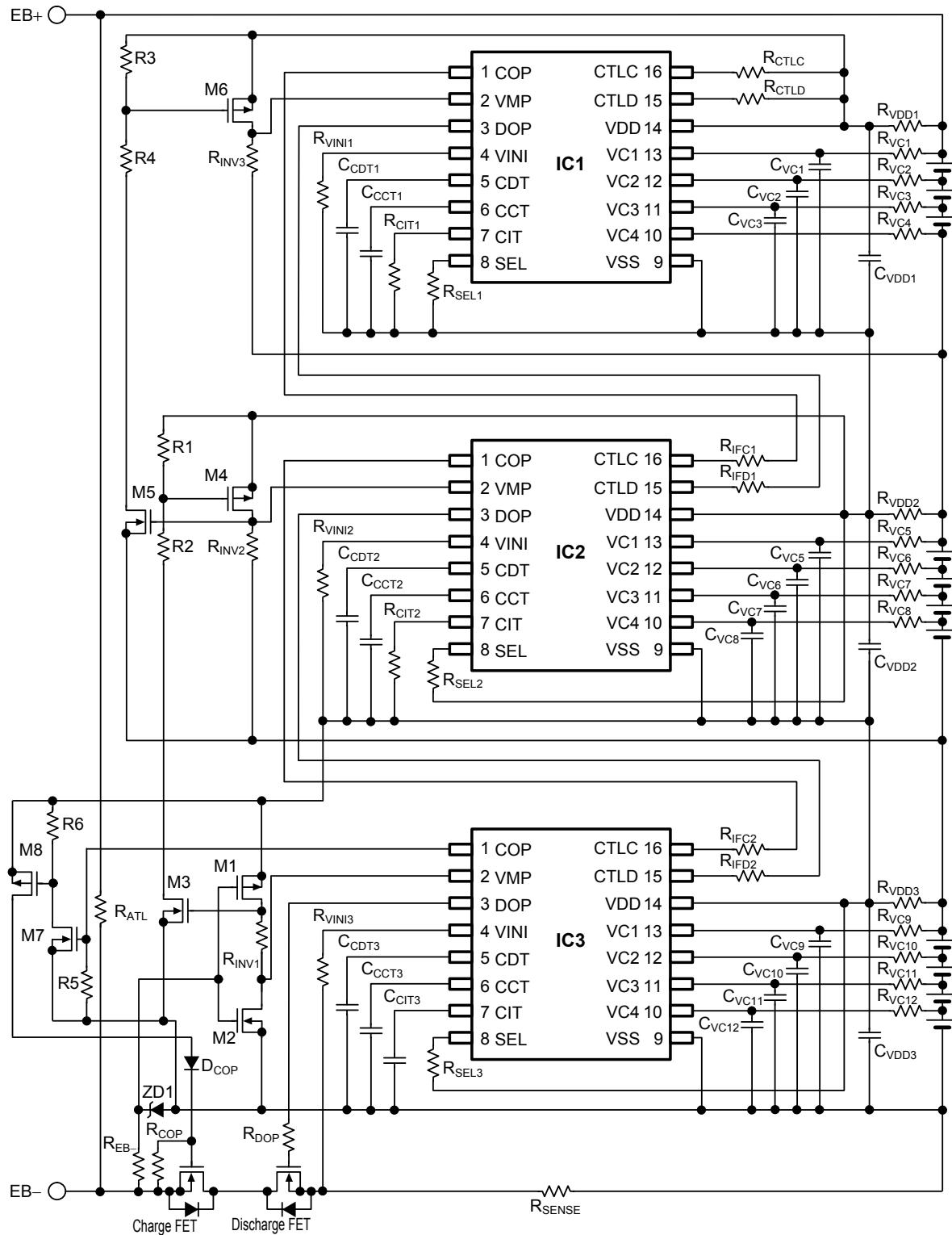3. 5 Protection circuit for 11-series cell (with discharge overcurrent protection function)



Remark Refer to "3. 9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.


Figure 15

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

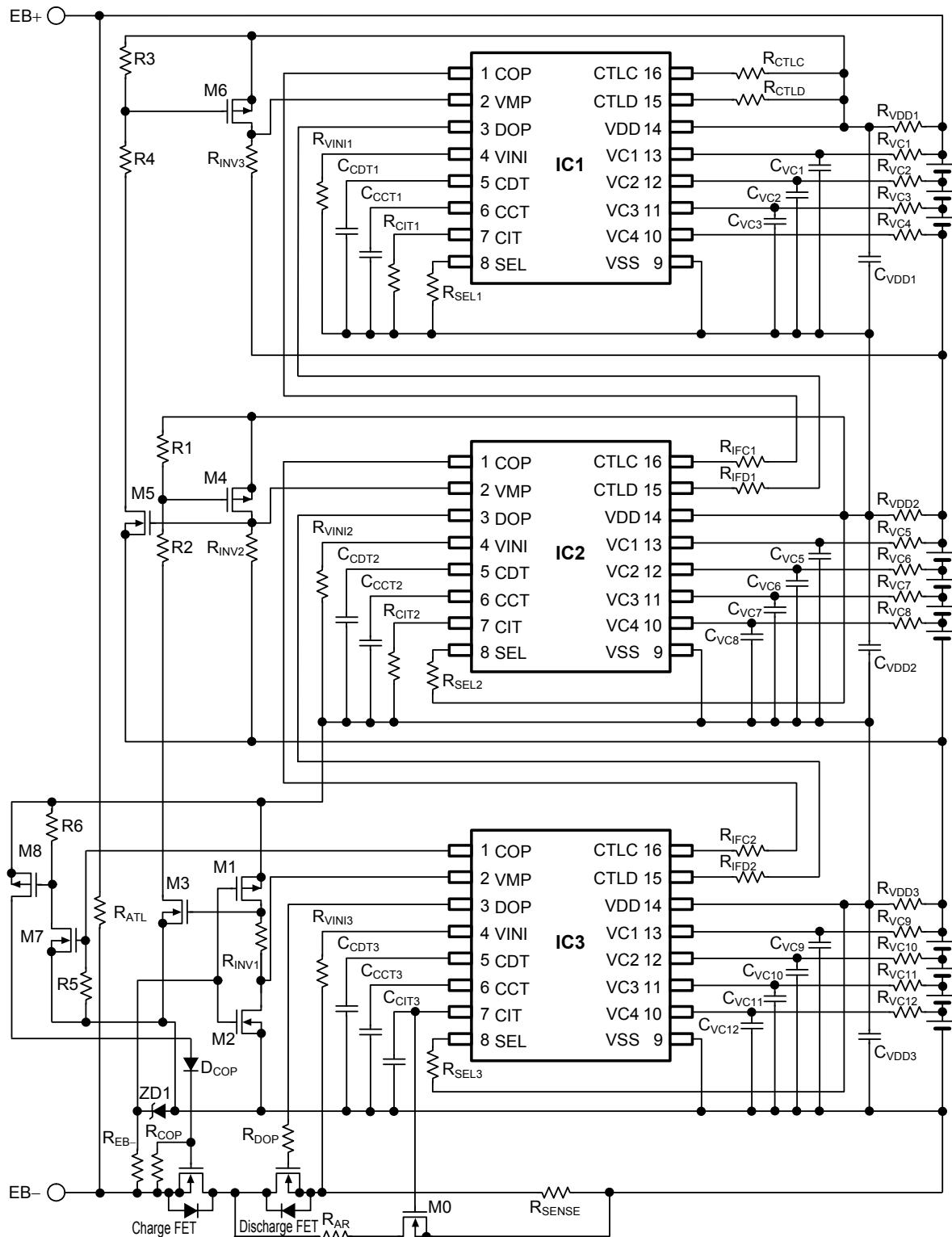3. 6 Protection circuit for 11-series cell

(with discharge overcurrent protection function and automatic recovery function)




Remark Refer to "3. 9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.

Figure 16

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

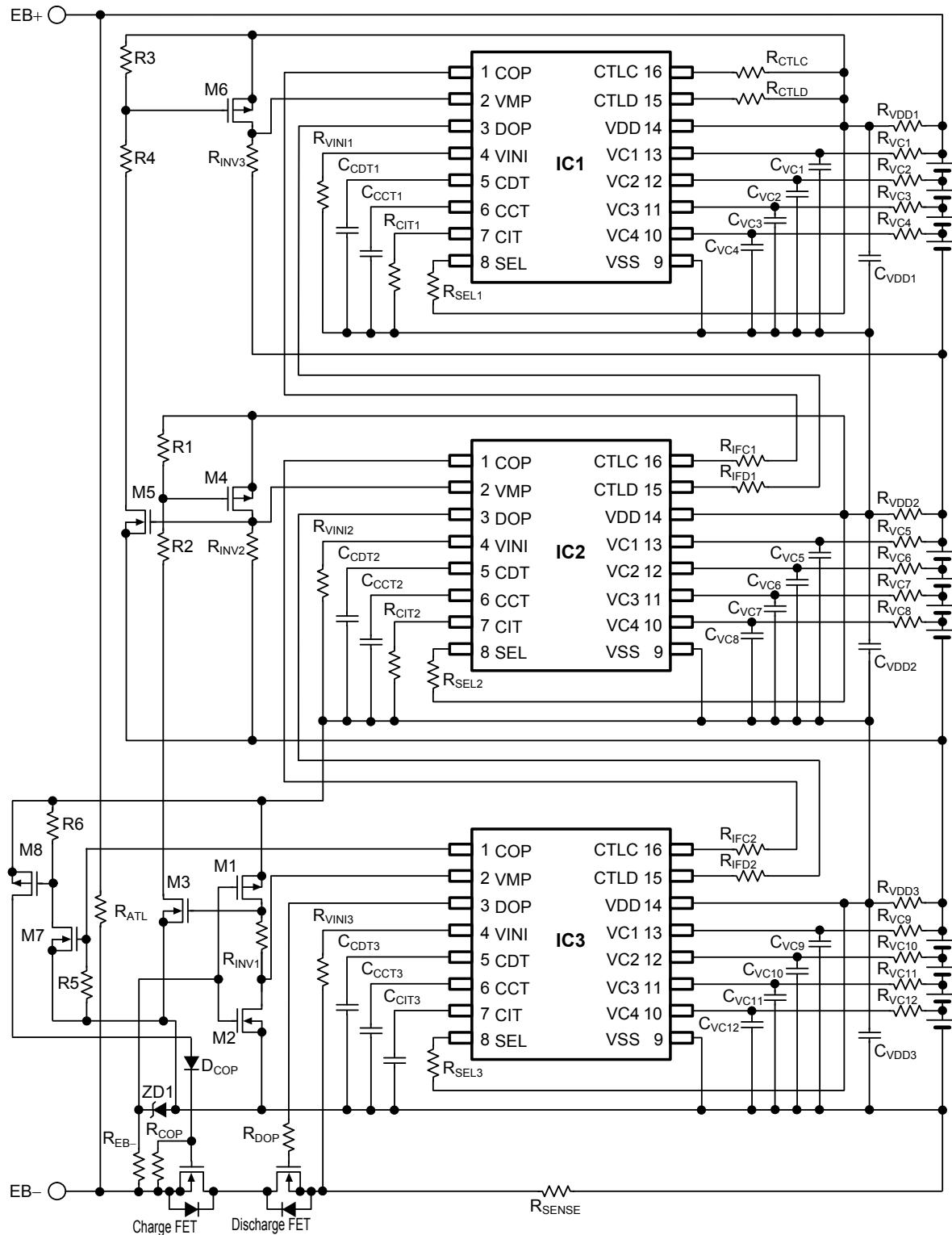3.7 Protection circuit for 12-series cell (with discharge overcurrent protection function)




Remark Refer to "3.9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.

Figure 17

- Caution 1.** The above connection example may be changed without notice.
2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

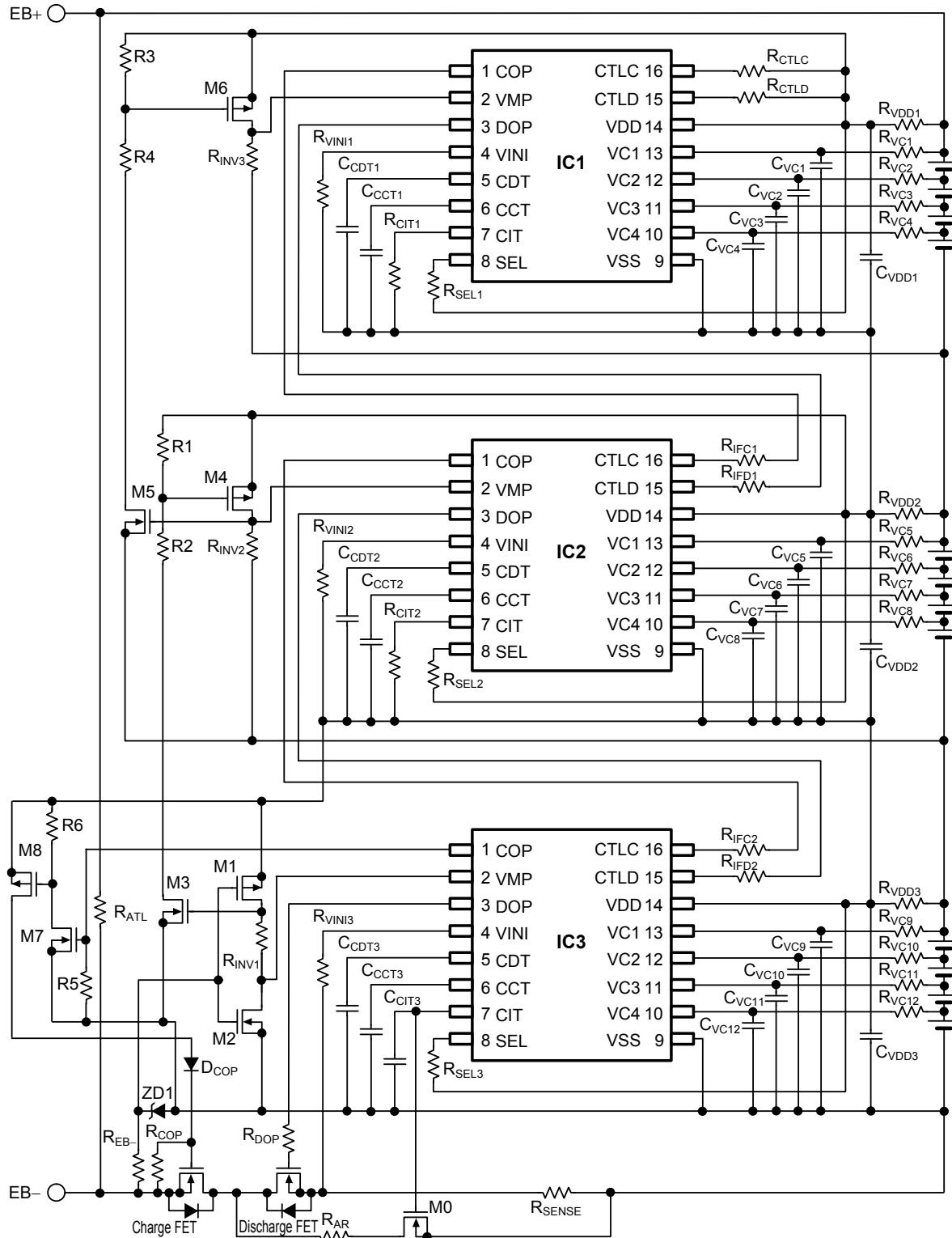**3.8 Protection circuit for 12-series cell
(with discharge overcurrent protection function and automatic recovery function)**



Remark Refer to "3.9 External components list (Protection circuit for 9-series to 12-series cell)" for constants of external components.

Figure 18

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

3. 9 External components list (Protection circuit for 9-series to 12-series cell)

Table 3 shows external components in the connection examples of Figure 11 to Figure 18.

Table 3 (1 / 2)

Symbol	Typical	Unit	Components Name	Maker	Note
IC1	–	–	S-8204B	ABLIC Inc.	Necessary
IC2	–	–	S-8204B	ABLIC Inc.	Necessary
IC3	–	–	S-8204B	ABLIC Inc.	Necessary
R _{VC1}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC2}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC3}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC4}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC5}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC6}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC7}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC8}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC9}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC10}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC11}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VC12}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
C _{VC1}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC2}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC3}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC4}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC5}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC6}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC7}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC8}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC9}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC10}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC11}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VC12}	0.047	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
R _{VDD1}	47	Ω	MCR03	ROHM CO., LTD.	Recommend
R _{VDD2}	47	Ω	MCR03	ROHM CO., LTD.	Recommend
R _{VDD3}	47	Ω	MCR03	ROHM CO., LTD.	Recommend
C _{VDD1}	1	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VDD2}	1	μF	GRM188B	Murata Manufacturing Co., Ltd.	Recommend
C _{VDD3}	1.5	μF	GRM32D	Murata Manufacturing Co., Ltd.	Recommend
R _{SEL1}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{SEL2}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{SEL3}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
C _{CCT1}	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
C _{CCT2}	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
C _{CCT3}	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
C _{CDT1}	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
C _{CDT2}	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
C _{CDT3}	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–
R _{CIT1}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{CIT2}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
C _{CIT3}	0.1	μF	GRM188B	Murata Manufacturing Co., Ltd.	–

Table 3 (2 / 2)

Symbol	Typical	Unit	Components Name	Maker	Note
R _{VINI1}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VINI2}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{VINI3}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{CTLC}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{CTLD}	1	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{IFC1}	5.1	MΩ	MCR03	ROHM CO., LTD.	Necessary
R _{IFD1}	5.1	MΩ	MCR03	ROHM CO., LTD.	Necessary
R _{IFC2}	5.1	MΩ	MCR03	ROHM CO., LTD.	Necessary
R _{IFD2}	5.1	MΩ	MCR03	ROHM CO., LTD.	Necessary
R _{INV1}	5.1	kΩ	MCR03	ROHM CO., LTD.	Necessary
R _{INV2}	1	MΩ	MCR03	ROHM CO., LTD.	Recommend
R _{INV3}	1	MΩ	MCR03	ROHM CO., LTD.	Recommend
R _{COP}	1	MΩ	MCR03	ROHM CO., LTD.	Recommend
R _{DOP}	51	kΩ	MCR03	ROHM CO., LTD.	Recommend
D _{COP}	—	—	1SS355	ROHM CO., LTD.	Recommend
R _{SENSE}	—	—	—	—	—
M0	—	—	1HN04CH	ON Semiconductor	Recommend
M1	—	—	2SJ210C	Renesas Electronics Corporation	Recommend
M2	—	—	2SK1590C	Renesas Electronics Corporation	Recommend
M3	—	—	2SK1590C	Renesas Electronics Corporation	Recommend
M4	—	—	2SJ210C	Renesas Electronics Corporation	Recommend
M5	—	—	2SK1590C	Renesas Electronics Corporation	Recommend
M6	—	—	2SJ210C	Renesas Electronics Corporation	Recommend
M7	—	—	2SK1590C	Renesas Electronics Corporation	Recommend
M8	—	—	1HP04CH	ON Semiconductor	Recommend
ZD1	—	—	UDZS18B	ROHM CO., LTD.	Recommend
R1	10	MΩ	MCR03	ROHM CO., LTD.	Recommend
R2	10	MΩ	MCR03	ROHM CO., LTD.	Recommend
R3	10	MΩ	MCR03	ROHM CO., LTD.	Recommend
R4	10	MΩ	MCR03	ROHM CO., LTD.	Recommend
R5	5.1	MΩ	MCR03	ROHM CO., LTD.	Recommend
R6	5.1	MΩ	MCR03	ROHM CO., LTD.	Recommend
R _{AR}	100	kΩ	MCR03	ROHM CO., LTD.	Recommend
R _{EB-}	1	MΩ	MCR03	ROHM CO., LTD.	Necessary
R _{ATL}	20	MΩ	MCR03	ROHM CO., LTD.	Recommend
Charge FET	—	—	—	—	—
Discharge FET	—	—	—	—	—

Caution 1. The above constants are subject to change without prior notice.

2. These constants will not guarantee successful operation. Perform thorough evaluation using the actual application to set the constants.

4. Withstand voltage protection when S-8204B Series devices are connected in cascade

The S-8204B Series can be used as a battery protection circuit for multi-series cell through cascade connection. However, the S-8204B Series may be damaged when it is exposed to voltage exceeding the absolute maximum ratings, resulting from the external components in this type of circuit design.

The potential for damage exists during battery connection under the following conditions:

- When the connecting of each cell is out of turn.
- In case that there is a difference at the time when each cell and each pin of the protection board are connected by using a connector in the application circuit where a cell of protection board is connected with a cell, as shown in **Figure 19**.

In order to prevent the destruction to the S-8204B Series, it is recommended to add the Zener diode of 20 V to 22 V between the VDD pin and the VSS pin of the S-8204B Series beforehand, as shown in **Figure 19**.

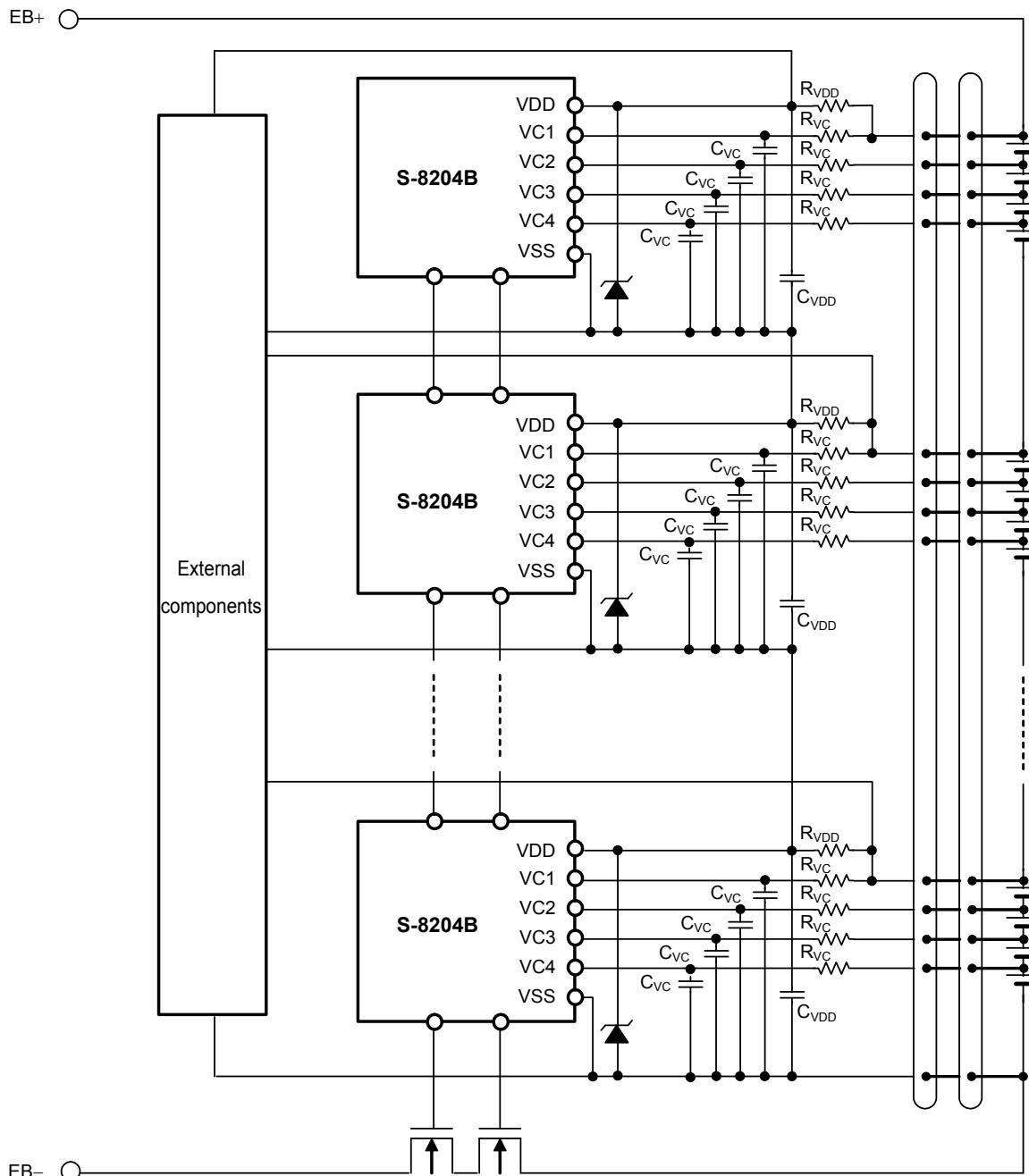


Figure 19

Caution 1. The above connection example may be changed without notice.

2. It has not been confirmed whether the operation is normal or not in circuits other than the above example of connection. The example of connection shown above will not guarantee successful operation.

5. Precautions

- The usage described in this application note is typical examples using ICs of ABLIC Inc.
Perform thorough evaluation before use.
- When designing for mass production using an application circuit described herein, the product deviation and temperature characteristics of the external components should be taken into consideration. ABLIC Inc. shall not bear any responsibility for patent infringements related to products using the circuits described herein.
- ABLIC Inc. claims no responsibility for any disputes arising out of or in connection with any infringement by products including this IC of patents owned by a third party.

6. Related source

Refer to the following datasheet for details of the S-8204B Series.

S-8204B Series Datasheet

The information described herein is subject to change without notice.

Regarding the newest version, contact our sales office.

Select product category and product name on our website, download the PDF file.

www.ablic.com

[ABLIC Inc. website](http://www.ablic.com)

Disclaimers (Handling Precautions)

1. All the information described herein (product data, specifications, figures, tables, programs, algorithms and application circuit examples, etc.) is current as of publishing date of this document and is subject to change without notice.
2. The circuit examples and the usages described herein are for reference only, and do not guarantee the success of any specific mass-production design.
ABLIC Inc. is not liable for any losses, damages, claims or demands caused by the reasons other than the products described herein (hereinafter "the products") or infringement of third-party intellectual property right and any other right due to the use of the information described herein.
3. ABLIC Inc. is not liable for any losses, damages, claims or demands caused by the incorrect information described herein.
4. Be careful to use the products within their ranges described herein. Pay special attention for use to the absolute maximum ratings, operation voltage range and electrical characteristics, etc.
ABLIC Inc. is not liable for any losses, damages, claims or demands caused by failures and / or accidents, etc. due to the use of the products outside their specified ranges.
5. Before using the products, confirm their applications, and the laws and regulations of the region or country where they are used and verify suitability, safety and other factors for the intended use.
6. When exporting the products, comply with the Foreign Exchange and Foreign Trade Act and all other export-related laws, and follow the required procedures.
7. The products are strictly prohibited from using, providing or exporting for the purposes of the development of weapons of mass destruction or military use. ABLIC Inc. is not liable for any losses, damages, claims or demands caused by any provision or export to the person or entity who intends to develop, manufacture, use or store nuclear, biological or chemical weapons or missiles, or use any other military purposes.
8. The products are not designed to be used as part of any device or equipment that may affect the human body, human life, or assets (such as medical equipment, disaster prevention systems, security systems, combustion control systems, infrastructure control systems, vehicle equipment, traffic systems, in-vehicle equipment, aviation equipment, aerospace equipment, and nuclear-related equipment), excluding when specified for in-vehicle use or other uses by ABLIC, Inc. Do not apply the products to the above listed devices and equipments.
ABLIC Inc. is not liable for any losses, damages, claims or demands caused by unauthorized or unspecified use of the products.
9. In general, semiconductor products may fail or malfunction with some probability. The user of the products should therefore take responsibility to give thorough consideration to safety design including redundancy, fire spread prevention measures, and malfunction prevention to prevent accidents causing injury or death, fires and social damage, etc. that may ensue from the products' failure or malfunction.
The entire system in which the products are used must be sufficiently evaluated and judged whether the products are allowed to apply for the system on customer's own responsibility.
10. The products are not designed to be radiation-proof. The necessary radiation measures should be taken in the product design by the customer depending on the intended use.
11. The products do not affect human health under normal use. However, they contain chemical substances and heavy metals and should therefore not be put in the mouth. The fracture surfaces of wafers and chips may be sharp. Be careful when handling these with the bare hands to prevent injuries, etc.
12. When disposing of the products, comply with the laws and ordinances of the country or region where they are used.
13. The information described herein contains copyright information and know-how of ABLIC Inc. The information described herein does not convey any license under any intellectual property rights or any other rights belonging to ABLIC Inc. or a third party. Reproduction or copying of the information from this document or any part of this document described herein for the purpose of disclosing it to a third-party is strictly prohibited without the express permission of ABLIC Inc.
14. For more details on the information described herein or any other questions, please contact ABLIC Inc.'s sales representative.
15. This Disclaimers have been delivered in a text using the Japanese language, which text, despite any translations into the English language and the Chinese language, shall be controlling.

2.4-2019.07